

وَمَا أُوتِيتُهُ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

---

## Analog IC Design

---

### Lecture 06 Basic Amplifier Stages

---

Dr. Hesham A. Omran

Integrated Circuits Laboratory (ICL)  
Electronics and Communications Eng. Dept.  
Faculty of Engineering  
Ain Shams University

# Outline

---

- Recapping previous key results
- Why amplifiers?
- Basic amplifier operation
- Basic amplifier analysis
- Rin/out shortcuts
  - Looking from drain
  - Looking from source
- GmRout method
- Basic amplifier topologies
  - Common Source (CS)
  - Common Gate (CG)
  - Common Drain (CD) – Source Follower (SF)
- Large signal behavior

# Outline

---

- Recapping previous key results
- Why amplifiers?
- Basic amplifier operation
- Basic amplifier analysis
- Rin/out shortcuts
  - Looking from drain
  - Looking from source
- GmRout method
- Basic amplifier topologies
  - Common Source (CS)
  - Common Gate (CG)
  - Common Drain (CD) – Source Follower (SF)
- Large signal behavior

# MOSFET in Saturation




- The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

$$V_{GD} \leq V_{TH} \text{ OR } V_{DS} \geq V_{ov}$$


- Square-law (long channel MOS)

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$
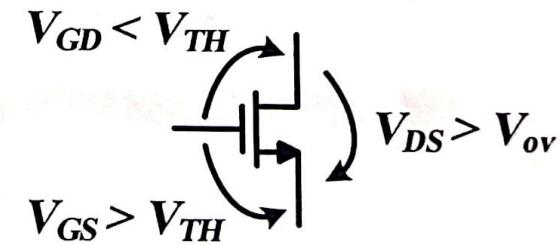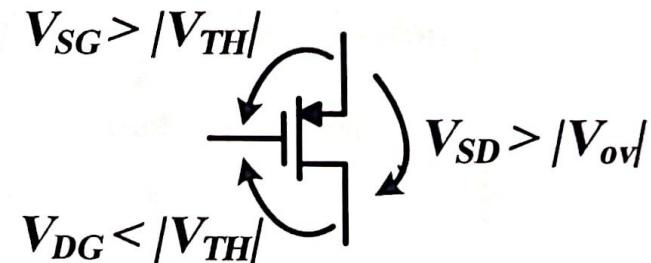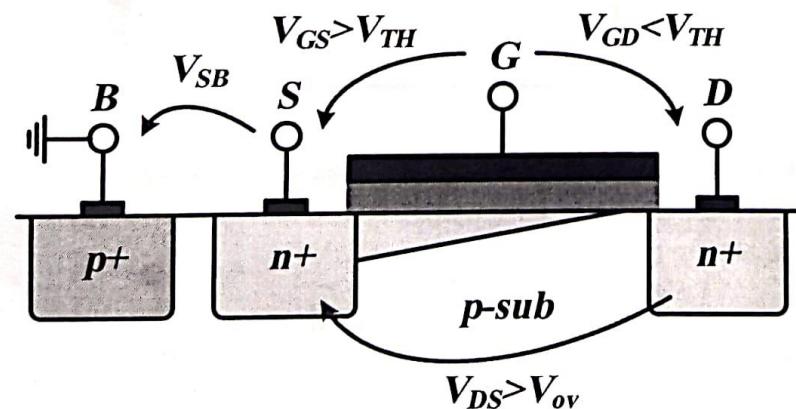
$$V_{SB} \uparrow \Rightarrow V_{TH} \uparrow$$




# Regions of Operation Summary

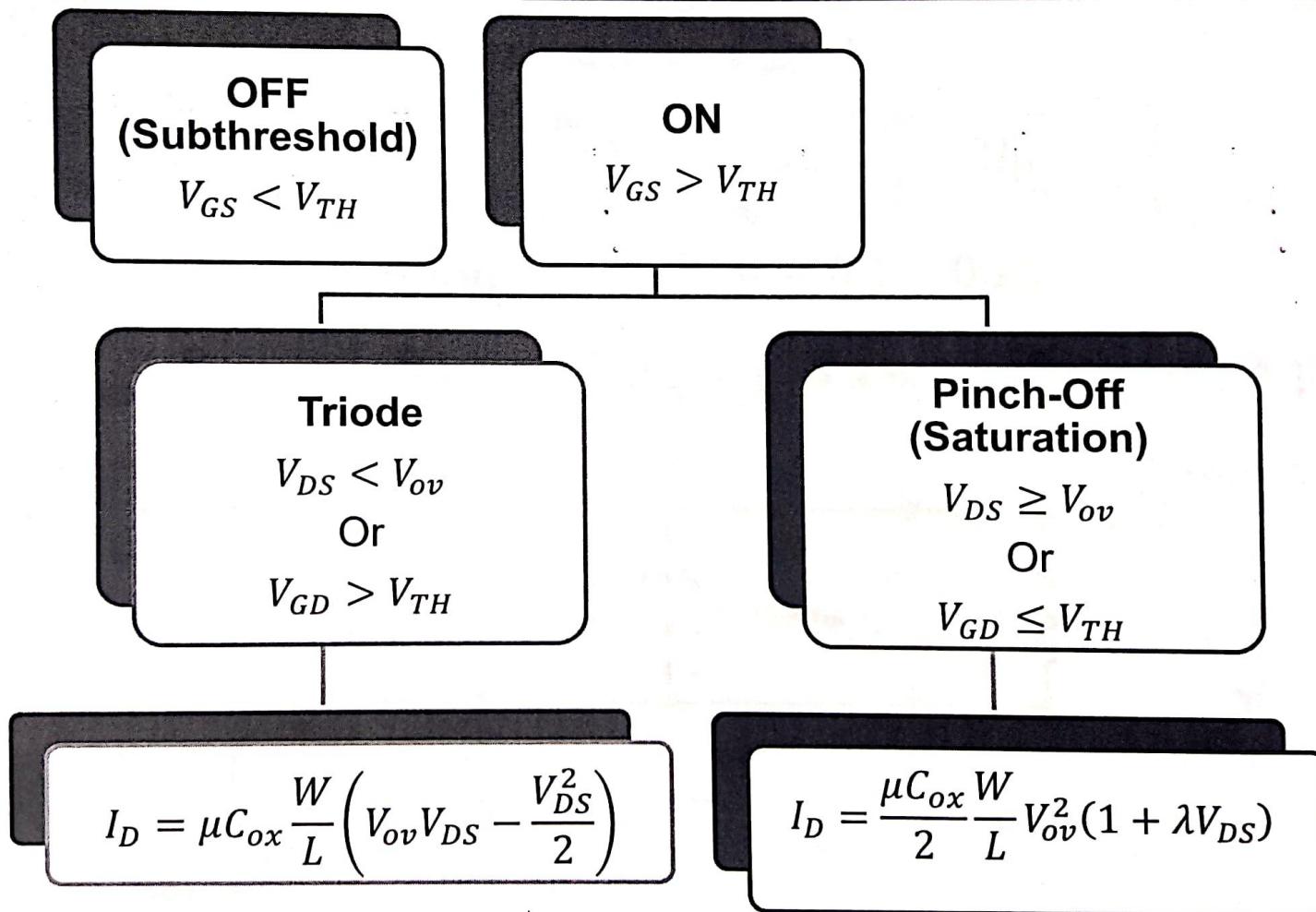
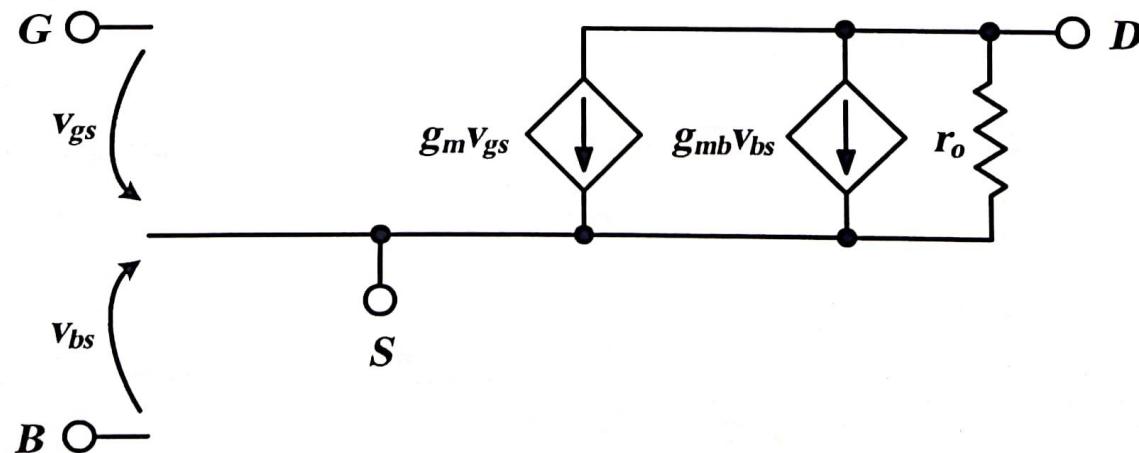
# Low-Frequency Small-Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$
$$g_{mb} = \eta g_m \quad \eta \approx 0.1 - 0.25$$

$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{V_A}{I_D} = \frac{1}{\lambda I_D} \quad V_A \propto L \leftrightarrow \lambda \propto \frac{1}{L} \quad V_{DS} \uparrow V_A \uparrow$$




# Outline

---

- Recapping previous key results
- Why amplifiers?
- Basic amplifier operation
- Basic amplifier analysis
- $R_{in}/out$  shortcuts
  - Looking from drain
  - Looking from source
- $GmR_{out}$  method
- Basic amplifier topologies
  - Common Source (CS)
  - Common Gate (CG)
  - Common Drain (CD) – Source Follower (SF)
- Large signal behavior
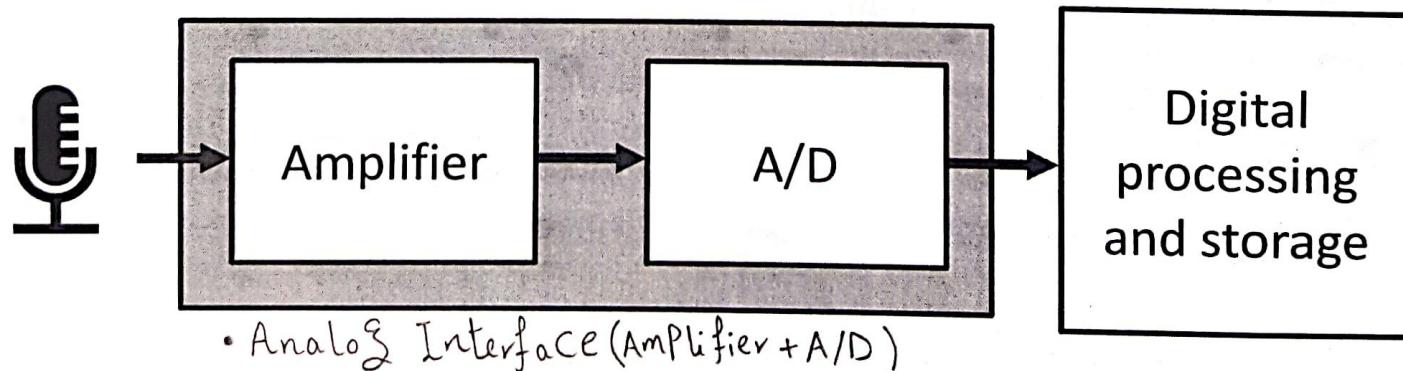
# Why Amplifiers?

- All the physical signals in the world around us are analog
  - Voice, light, temperature, pressure, etc. (wireless signals, electromagnetic waves)
- We (will) always need an “analog” interface circuit to connect between our physical world and our digital electronics
  - ★ Why Amplifiers?
    - ↳ it's used in Power management not only interfaces
- The physical signals are usually very weak
  - They must be amplified before any kind of processing
- Amplifiers are also needed in many other applications




## 06: Basic Amplifier Stages

★ On the other hand : When we learn how to design amplifiers we will learn all the important concepts in analog design (small signal model, frequency response, stability, feedback, etc.) many concepts we will learn in the context of the amplifiers but we will benefit from them while designing any analog block.

# Basic MOSFET Amplifier Topologies

- Common between i/P & o/P


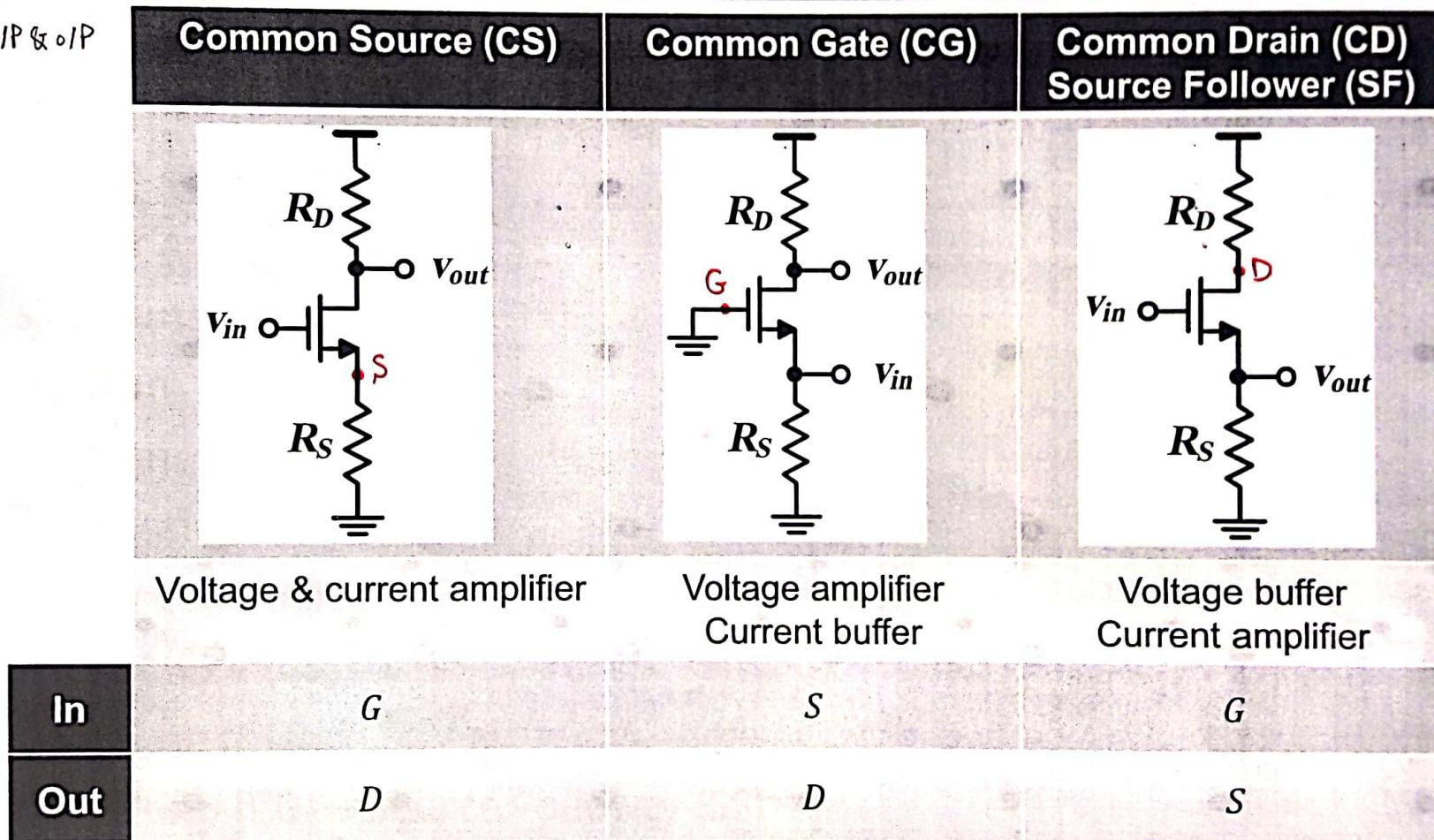


# Outline

---

- Recapping previous key results
- Why amplifiers?
- Basic amplifier operation
- Basic amplifier analysis
- Rin/out shortcuts
  - Looking from drain
  - Looking from source
- GmRout method
- Basic amplifier topologies
  - Common Source (CS)
  - Common Gate (CG)
  - Common Drain (CD) – Source Follower (SF)
- Large signal behavior

# CS Amplifier Example

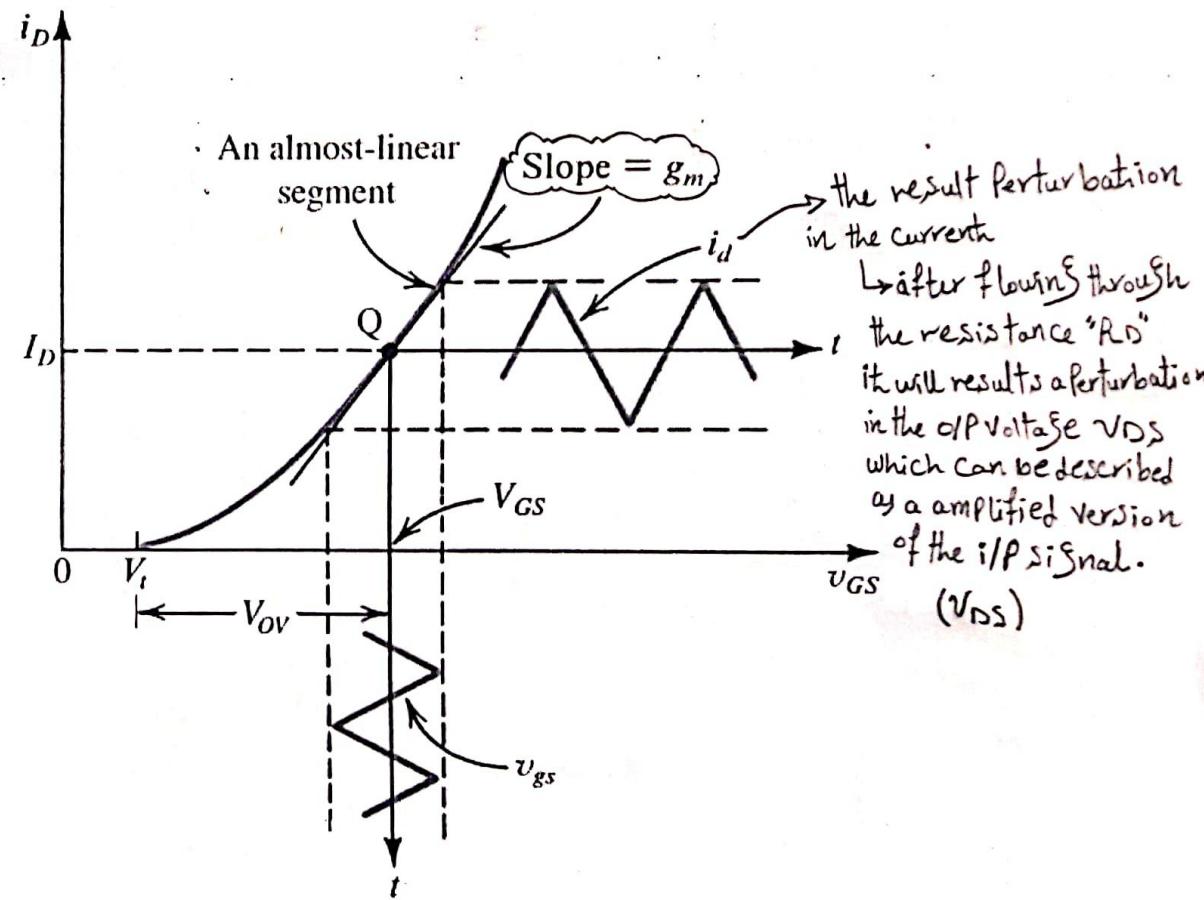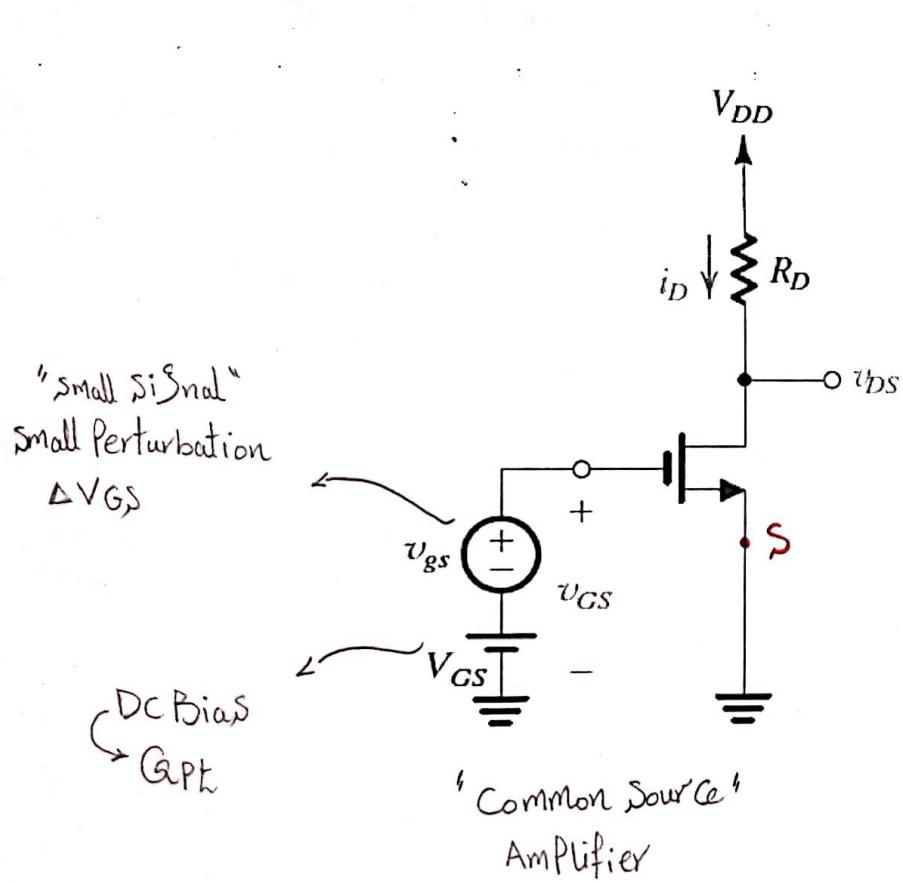

# CS Amplifier Example


\* There is a "180°-Phase shift" between the o/P & i/P, Why?

By increasing  $v_{GS} \uparrow$  then  $i_D \uparrow$  will increase making the voltage drop on  $R_D \uparrow$  which will results that the voltage  $V_{DS}$ ;  $V_{O/P}$ ; will decreases.

$$V_{DS} = V_{DD} - i_D \cdot R_D$$



const.

$\propto v_{GS}$ ; i/p;

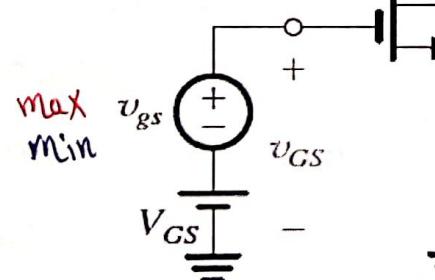

$$i_D \downarrow \quad R_D \quad \nabla_{RD}$$

$v_{DS}$   
min  
max

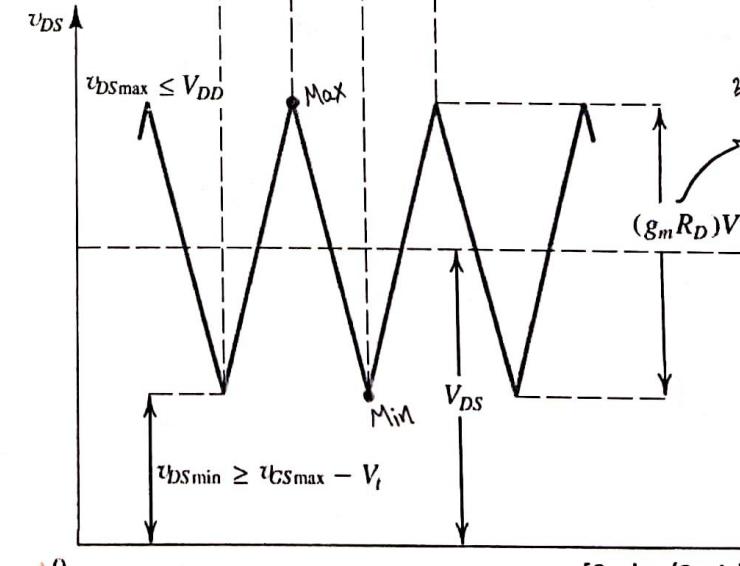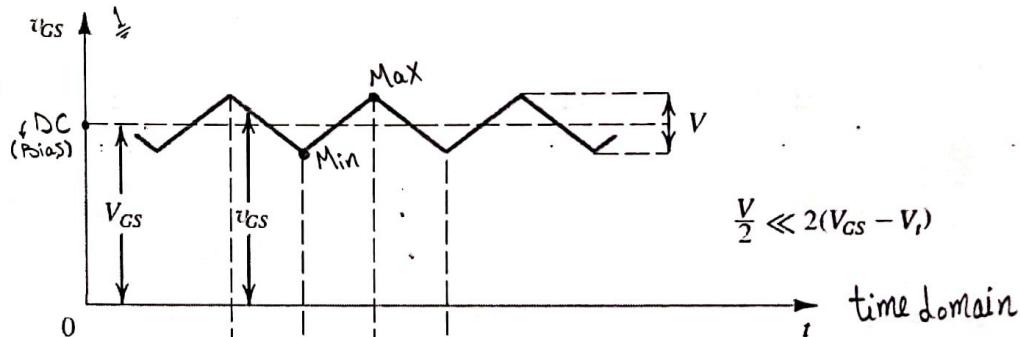

# Outline

---

- Recapping previous key results
- Why amplifiers?
- Basic amplifier operation
- Basic amplifier analysis
- Rin/out shortcuts
  - Looking from drain
  - Looking from source
- GmRout method
- Basic amplifier topologies
  - Common Source (CS)
  - Common Gate (CG)
  - Common Drain (CD) – Source Follower (SF)
- Large signal behavior

# Amplifier Analysis Steps


## 1. DC analysis

- Coupling and bypass capacitors  $\rightarrow$  open-circuit (o.c)  $\star X_C = \frac{1}{\omega C}$ , for  $DC \rightarrow \omega = 0 \therefore X_C = \frac{1}{0} = \infty$
- Calculate Q-point and check operation in saturation ( $V_{DS} > V_{ov}$ )

## 2. Calculate small signal parameters ( $g_m, r_o$ ) $\star (I_D) : \text{calculated from DC-Analysis}$ $\star \text{If DC Analysis is wrong} \therefore \text{The whole analysis will be wrong.}$
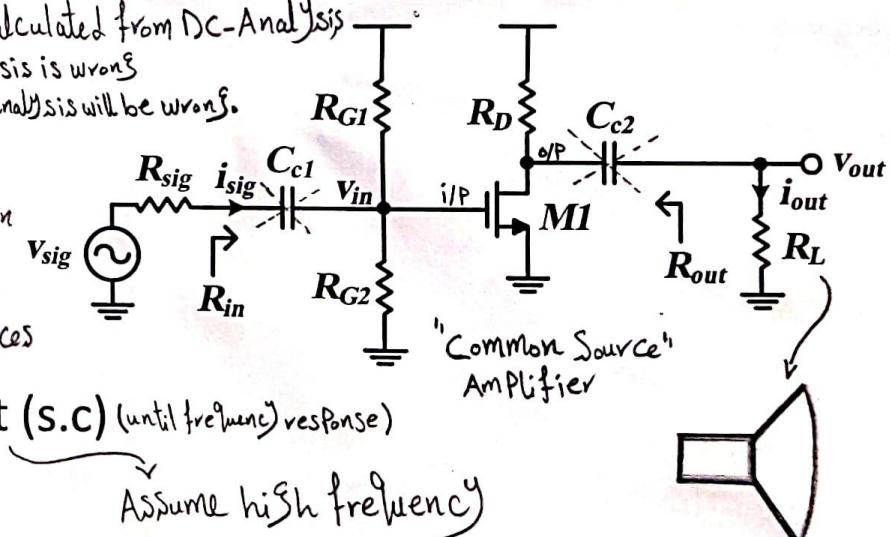
## 3. Draw the small signal equivalent circuit


- DC voltage source  $\rightarrow$  short-circuit (s.c.)  $\star$  Deactivation for all DC Sources
- DC current source  $\rightarrow$  open-circuit (o.c.)
- Coupling and bypass capacitors  $\rightarrow$  short-circuit (s.c) (until frequency response)


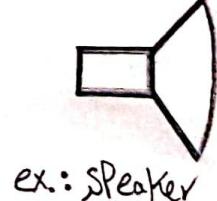
## 4. Determine the amplifier parameters (4 Parameters)

- Input resistance and output resistance
- Voltage gain and current gain

$$\therefore X_C = \frac{1}{\omega C \uparrow \uparrow}$$



3.1  $\star$  We don't amplify the battery we amplify a small signal which is on the input port of the amplifier (ex. signal from a microphone) we give it power to be amplified and come from the output port, this power comes from the battery.

# Amplifier Parameters

$$\square \quad R_{in} = \frac{v_{in}}{i_{in}} = \frac{v_{in}}{i_{sig}} \quad \text{Ohm's law}$$

independent source

□  $R_{out} = \frac{v_x}{i_x}$  @  $v_{sig} = 0$

1-  $R_{in}$ : is the resistance you will see when you look from the input Port

2-  $R_{out}$ : is like Norton or Thevenin resistance, we first deactivate all the independent sources (only one ' $V_{S1/S2}$ '), but where is the dependent source? -MOSFET, then imagine you put a voltage source ' $V_x$ ' @ o/P Port. This voltage source will generate current  $i_x \rightarrow R_{out} = \frac{V_x}{i_x}$

**3.**  **Voltage gain** =  $A_v = \frac{v_{out}}{v_{sig}} = \frac{v_{in}}{v_{sig}} \cdot \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_{sig} + R_{in}} \cdot \frac{v_{out}}{v_{in}}$

- The most important Parameter
- The signal we want to amplify
- ohm's law

- The most important Parameter

- The signal  $\leftarrow$   
we want to amplify

Current gain =  $A_i = \frac{i_{out}}{i_{sig}} = \frac{v_{out}/R_L}{v_{in}/R_{in}} = \frac{v_{out}}{v_{in}} \cdot \frac{R_{in}}{R_L}$


4-  $i_{out}$ : is the current flow  
the load can be the Speaker  
the sound we want to amplify

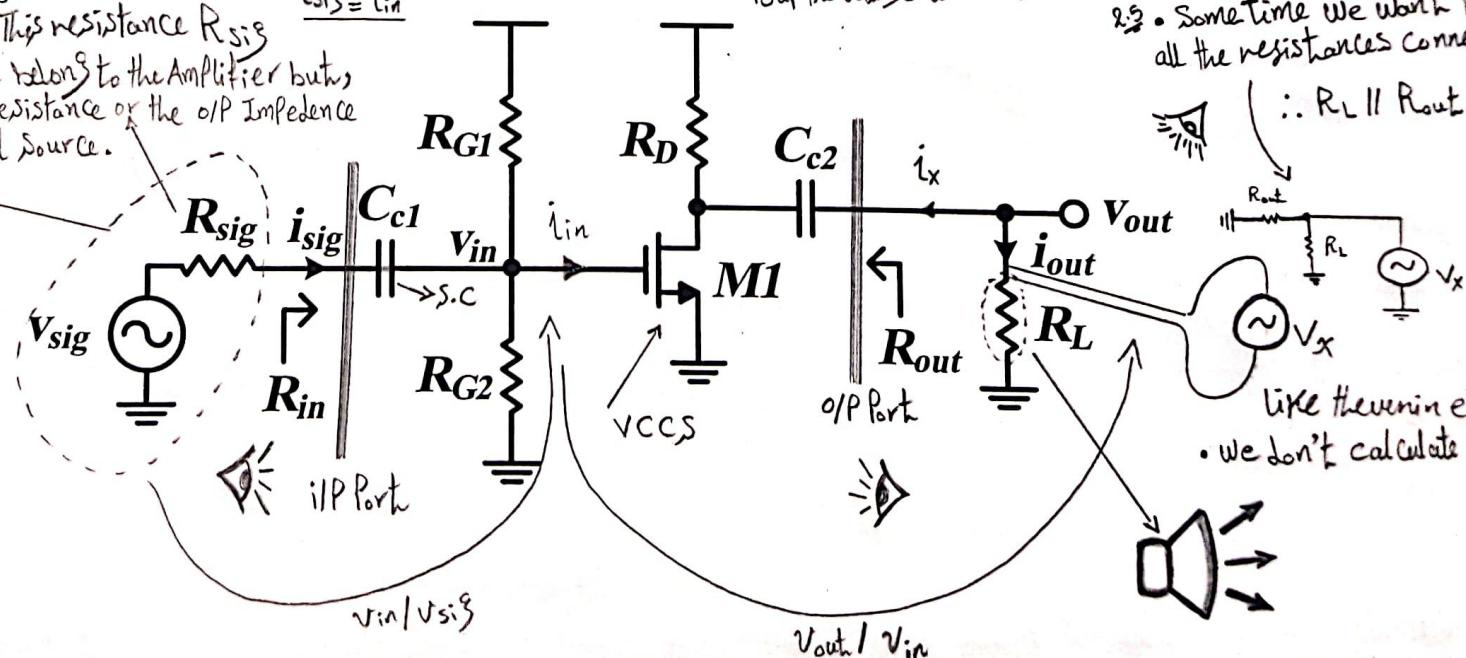3. You tell us before that the input resistance of the MOSFET is infinity, don't you? - Yes but it depends on the circuit. In this circuit it's not infinity (> It tells you) it is  $R_{\text{in}} = R_{\text{G}1} \parallel R_{\text{G}2}$ . Actually what differ from one amplifier to another is  $R_{\text{in}}$  equation. Voltage divider doesn't change.

• Sometimes we want to calculate all the resistances connected to the o/p



It is the o/p resistance or the o/p Impedance of the Signal Source.



like thevenin equivalent  
we don't calculate  $R_L$

# Large and Small Signal Analysis

	Large Signal Analysis	Small Signal Analysis
Model	Large signal model	Small signal model
Linearity	Non-linear (Square Law)	Linear
Simulation	DC and transient analysis ↳ simulation with time	AC analysis ↳ circuit response with frequency
Purpose	Calculate bias point, signal swing, distortion, etc. or slew rate ↳ transient	Calculate $A_v, R_{in}, R_{out}, BW$ , etc.
VDC	✓	S.C. } O.C. } Deactivation
IDC	✓	DC Sources
Capacitor	O.C. (in DC) $i = C \frac{dV}{dt}$ (in transient)	$1/\omega C$
Inductor	S.C. (in DC) $v = L \frac{di}{dt}$ (in transient)	$\omega L$ will be taken into consideration ↳ 'frequency Response'

- Differential equations are also reason to decrease the speed of the transient analysis.

\* Why Cap. & Ind. are O.C. & S.C. in DC but have value in Transient? - as DC is Const. Voltage then  $\frac{dV}{dt} = 0$ , but transient is Variable Voltage  
 ↳ ramp  $\sim V \sin$

# Amplifier Analysis Example

Assume biased in saturation unless otherwise stated.

But this don't underestimate the importance of biasing.  
if the Biasing is not correct everything will be wrong.  
↳ also in the simulation first thing to debug is the Bias Point.

$g_m r_o$  is the max gain that can be obtained from a single transistor: a.k.a. intrinsic gain

Practically: the Gain will be less than the intrinsic Gain


If we replace the current source with a resistor then

$$V_{out} = - (g_m V_{in}) \cdot (R_o / R_D) \quad \text{if } R_D \gg R_o$$

which will result smaller  $A_v$

∴ the ideal load in analog design is to use current source as it provides the max. possible gain  
by providing the needed current without reducing the resistance  
∴ without reducing the gain.

Very simple CS Amplifier

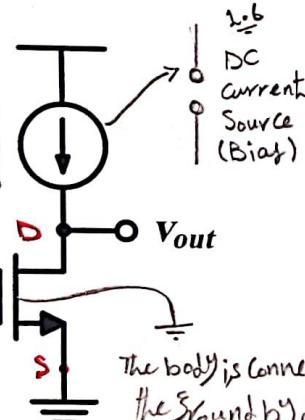

The body is connected to the ground by default (or it is not drawn)

∴ we wanna calculate the voltage gain.


$$V_{out} = -(g_m V_{in}) r_o, V_{in} = V_{gs}$$

$$\therefore |A_v| = \left| \frac{V_{out}}{V_{in}} \right| = g_m r_o$$

★  $g_m r_o$  "intrinsic Gain"  
one of the important parameters used when designing Analog Circuits.  
it is one of the "figures of merit".  
• figures of merit: numerical expression representing the performance or efficiency of a given device, material or procedure.

↳ connect every terminal in the box with that connected to it in the circuit.

in a Common Source amplifier

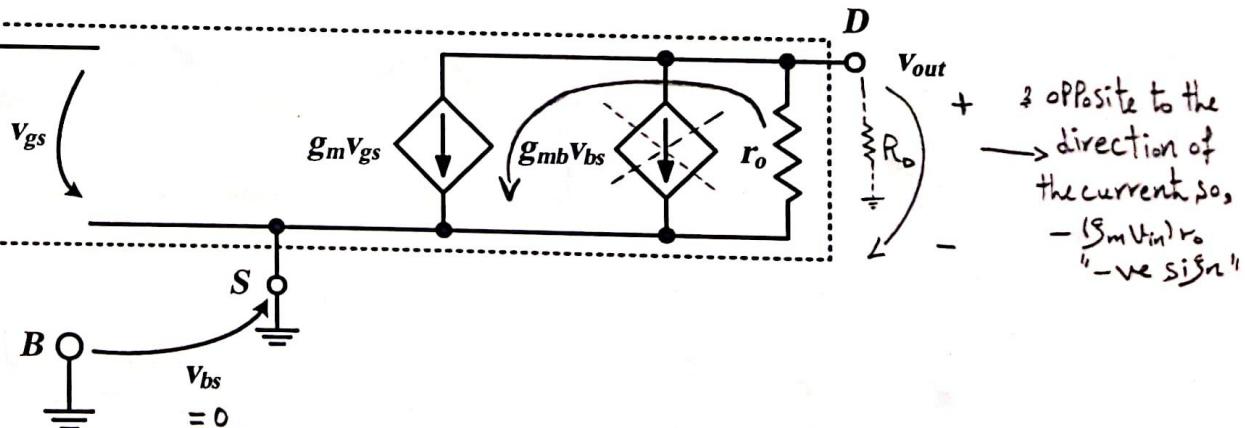


Opposite to the direction of the current so,  
 $-(g_m V_{in}) r_o$   
"negative sign"

\* one of the most important things you need to learn is the direct analysis on the schematics or if you have a circuit with 10 or 20 transistor it will be hard but impossible to replace each transistor and draw the model as it will take much time and you will probably go wrong
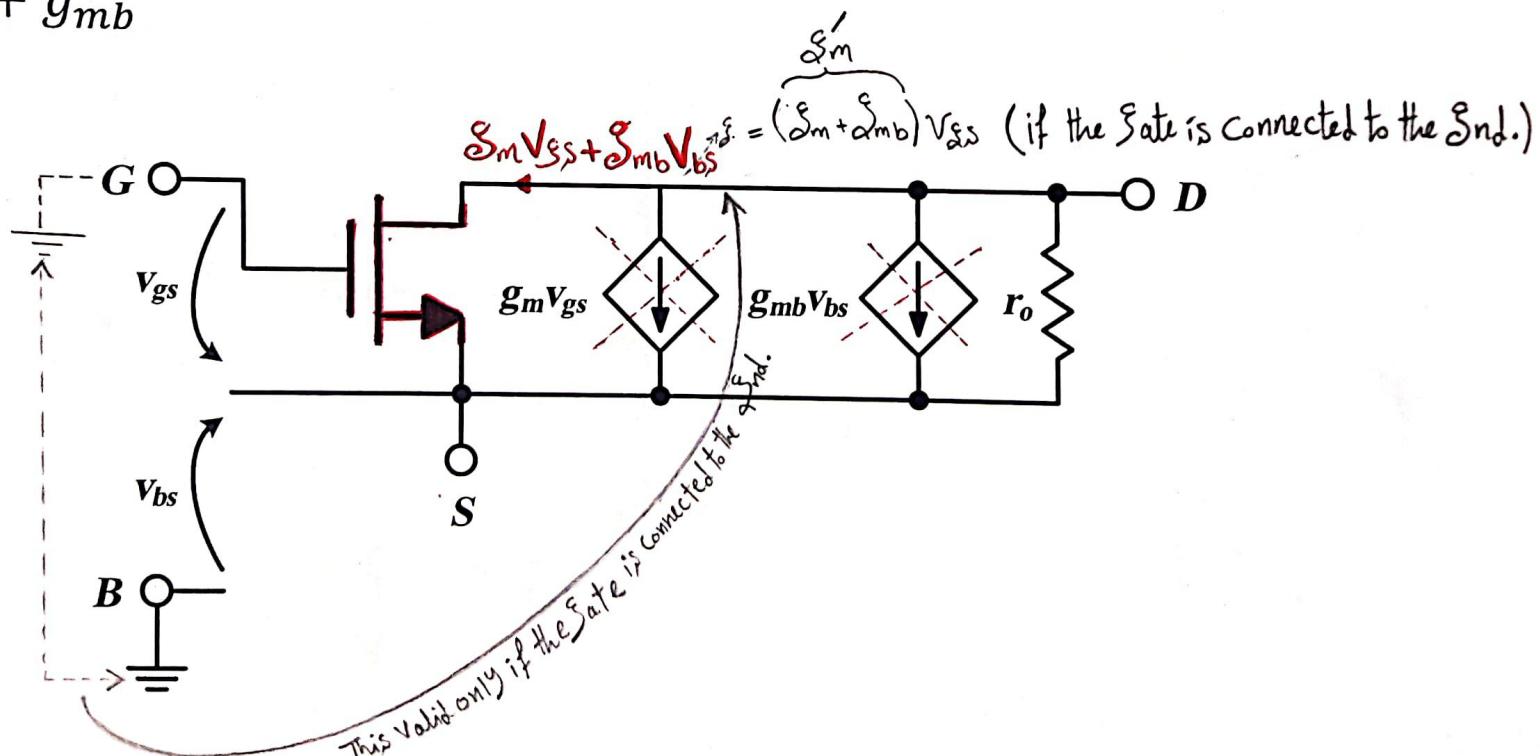
# Direct Analysis on Schematics


- No need to draw the small signal model every time
- Just remember we have two VCCSs and  $r_o$  between D and S
- If G is ac gnd, then  $v_{bs} = v_{gs} \rightarrow g_m$  and  $g_{mb}$  add
  - $g_m \rightarrow g_m + g_{mb}$

\* So, you should do the analysis direct on the schematic without drawing the equivalent circuit.


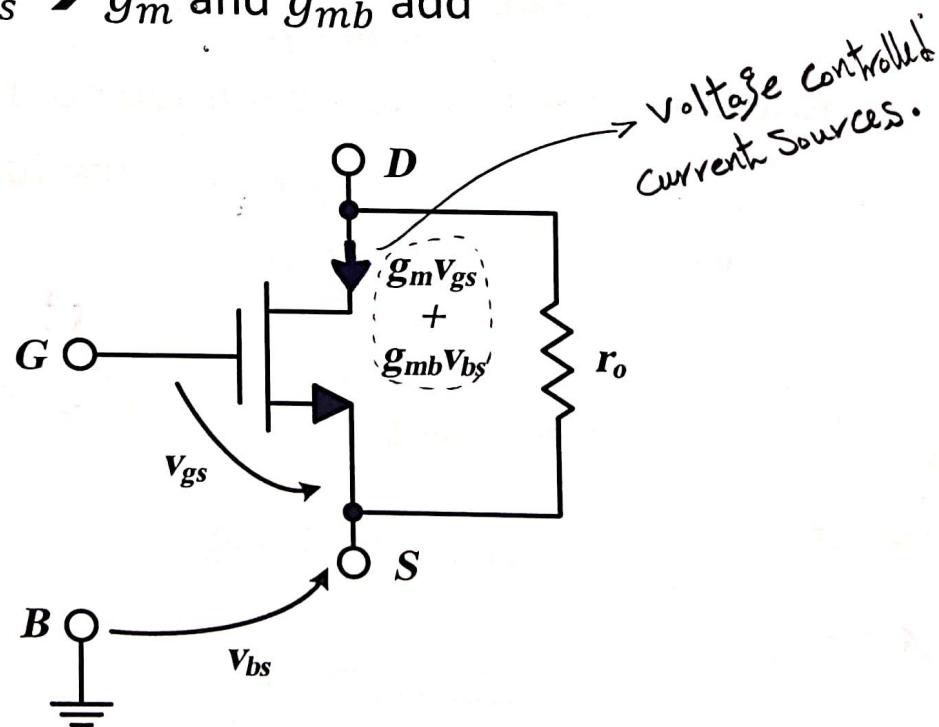
# Direct Analysis on Schematics

- No need to draw the small signal model every time
- Just remember we have two VCCSs and  $r_o$  between D and S
- If G is ac gnd, then  $v_{bs} = v_{gs} \rightarrow g_m$  and  $g_{mb}$  add
  - $g_m \rightarrow g_m + g_{mb}$



# Intrinsic Gain

$$\therefore v_{out} = -(g_m v_{in}) r_o$$

$$\therefore |A_v| = \left| \frac{v_{out}}{v_{in}} \right| = g_m r_o$$

- $g_m r_o$  is the max gain that can be obtained from a single transistor
- Common approximations that we usually use

① ex.  $\frac{1}{g_m} = 100\text{ k}\Omega$

→ how we considered this as a low value?  
• As it is a relative value you should compare it to  $r_o$  in the same circuit.

$$r_o = 10\text{ M}\Omega$$

$$\therefore 10\text{ M}\Omega \gg 100\text{ k}\Omega$$

$g_m r_o \gg 1$  \*The most important approximation we use in analog design.

$$r_o \gg \frac{1}{g_m}$$

"high" impedance ←      → "low" impedance

$$g_m + \frac{1}{r_o} \approx g_m$$


$$r_o // \frac{1}{g_m} \approx \frac{1}{g_m}$$

② In the Past technologies

$$g_m r_o > 100$$

> 50

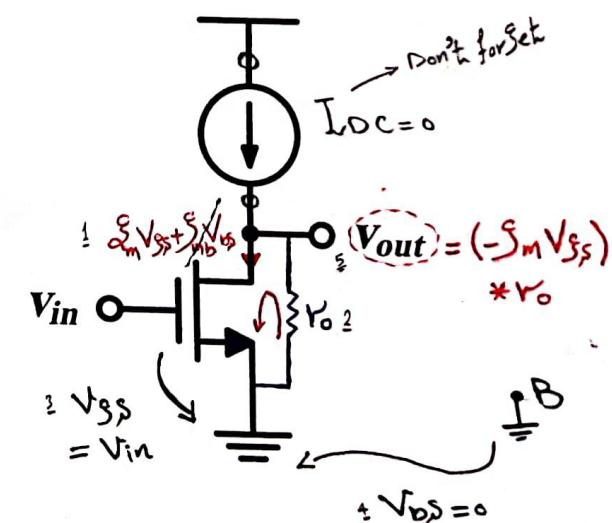so, these approximations were valid  
→ from the cons of the scaling down is that:  
 $g_m r_o < 10$  (intrinsic gain decreases)  
which makes some issues we will study later in the course




# Outline

---

- Recapping previous key results
- Why amplifiers?
- Basic amplifier operation
- Basic amplifier analysis
- Rin/out shortcuts
  - Looking from drain
  - Looking from source
- GmRout method
- Basic amplifier topologies
  - Common Source (CS)
  - Common Gate (CG)
  - Common Drain (CD) – Source Follower (SF)
- Large signal behavior
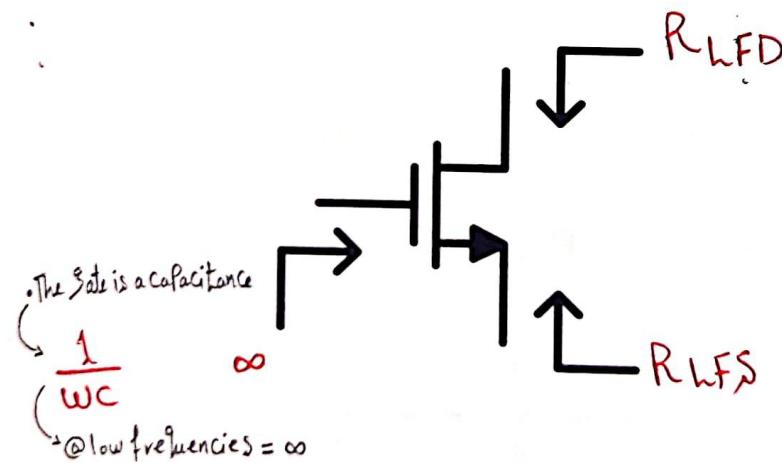
# Rin/out Shortcuts

- Find equivalent impedance looking from Gate, Source, and Drain



\*For BJT:

- You have to calculate  $R_{\text{Looking from Base}}$   
- as the base isn't open circuit.

# Looking From Drain

- If G is ac gnd, then  $v_{bs} = v_{gs} \rightarrow g_m$  and  $g_{mb}$  add
- $v_{gs} = -i_x R_S$  and  $g_m r_o \gg 1$
- Apply KCL at D

$$i_{in} = i_{out} @ D$$


$$i_x = (g_m + g_{mb})(-i_x R_S) + \frac{v_x - i_x R_S}{r_o}$$

*i<sub>x</sub> "Ohm's Law"*

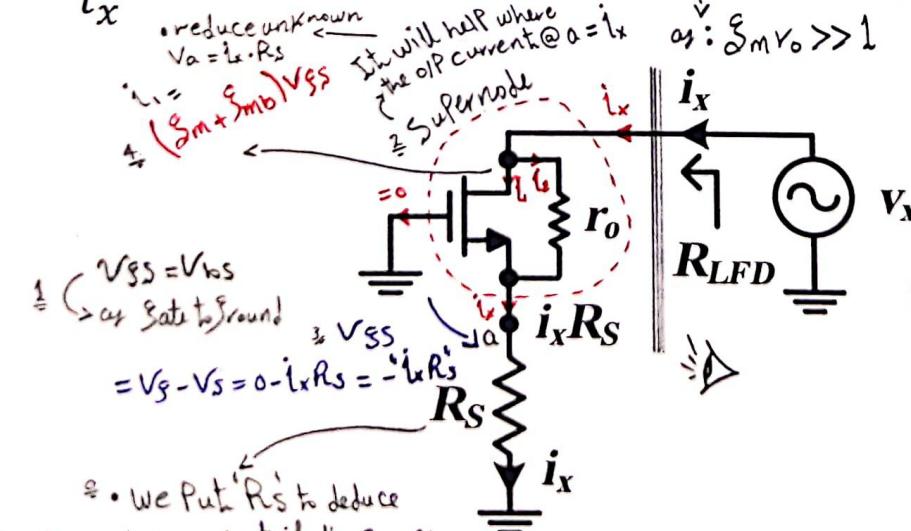4.5 \* If we put everything  
internally of  $V_x$  and  $i_x$  then  
the problem is solved.

$$R_{LFD} = \frac{v_x}{i_x} = r_o + [(g_m + g_{mb})r_o + 1]R_S \approx r_o[1 + (g_m + g_{mb})R_S]$$

\* It's useful to solve  
many unknowns as  
possible on the schematic  
without writing too many  
equations.



4.75 \* we can't neglect  $g_{mb}$   
as the source is floating not connected  
to the ground. ( $V_{SS} \neq 0$ )

$$R_{LFD} = \frac{V_x}{i_x}$$

\* We put 'R<sub>S</sub>' to deduce  
the general case, but if the source  
is to ground then put  $R_S = 0$   
→ Special Case

# Looking From Drain

$$\frac{1}{2} \left( R_{LFD} \approx r_o [1 + (g_m + g_{mb}) R_S] \right)$$



$$\frac{1}{2} * g_m r_o \gg 1$$

- <sup>3</sup>  Special case:  $R_S = 0$  (G and S ac s.c.)  $\rightarrow$  active load

$$R_{LFD} = r_o$$

- Drain is a high-impedance node (H.I.N.)

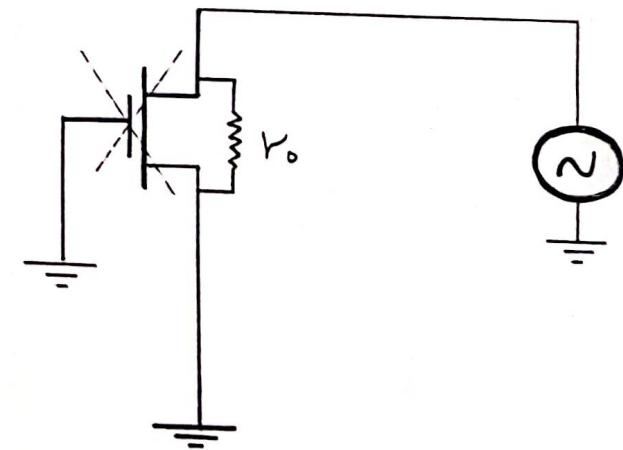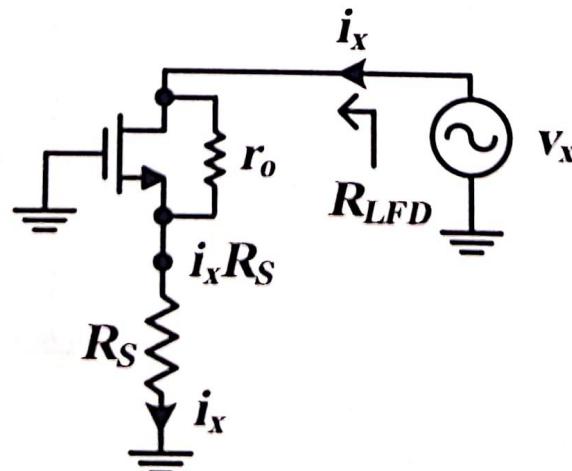$\hookrightarrow$  or if  $r_o$  has a value  $\Rightarrow R_{LFD} > r_o$   
 $\therefore R_{LFD}$  will be very high-impedance.




\*Why we called it active source?

- when  $R_S = 0$
- $\therefore V_{GS} = 0$
- MOSFET is basically (current source + output resistance)

$\rightarrow$  The Current Source ( $S_m V_{GS} + S_{mb} V_{DS}$ ) = zero

$\therefore$  The MOSFET will be only a resistance (load)  
 'Active load': active element but behave as a load.

# Active Load (Source OFF)

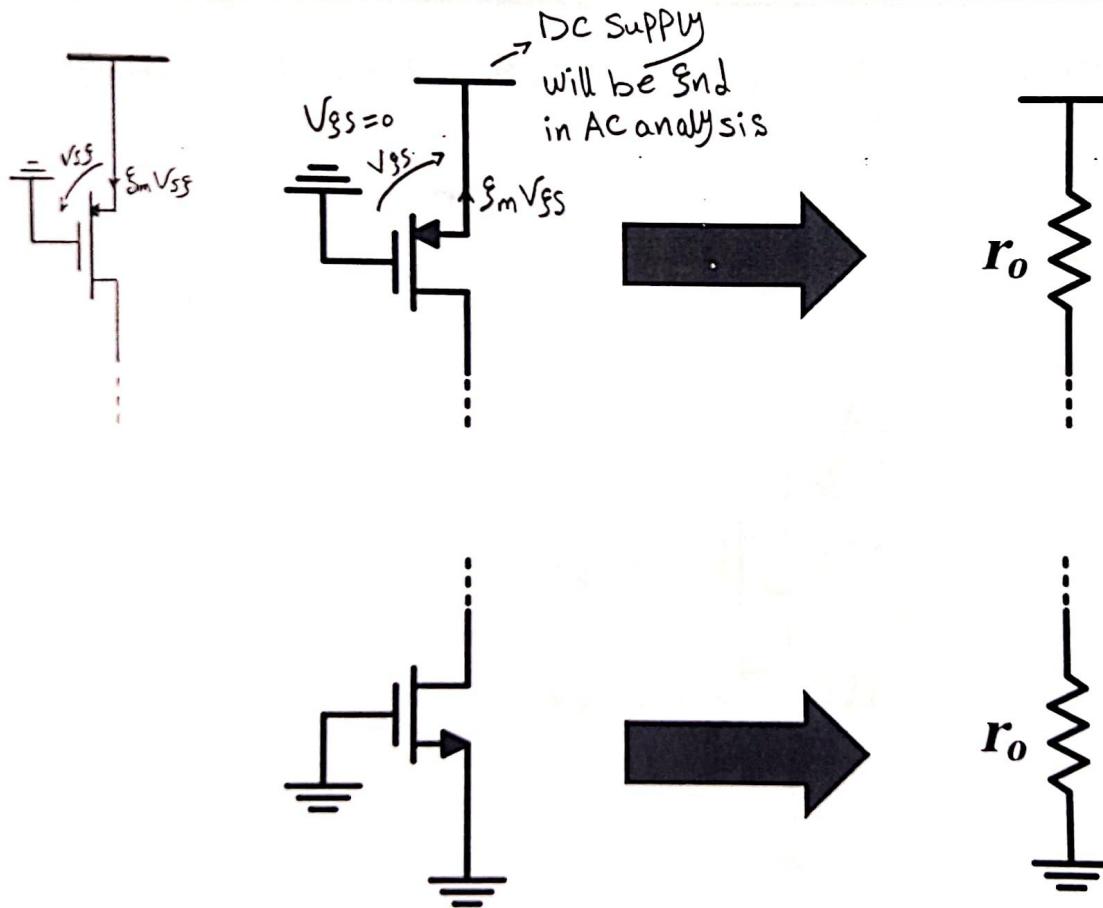


# Quiz

- Assume M1 and M2 have the same  $g_m$  and  $r_o$ ,  $g_m r_o \gg 1$ , and neglect body effect
  - Find  $R_X$       ~~DC Source~~      2. If T has two

$$R_{LFD} = R_o \left[ 1 + (\xi_m + \xi_{mb}) R_s \right]$$

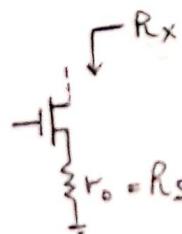
- for  $M_1$ :  $R_{LFD} = r_0$  (active load)



$$\therefore R_{LFD} = R_0 \left[ 1 + \left( \frac{S_m}{R_0} + \frac{S_{mb}}{R_0} \right) \right]$$

$$\therefore \delta m r_0 \gg 1$$

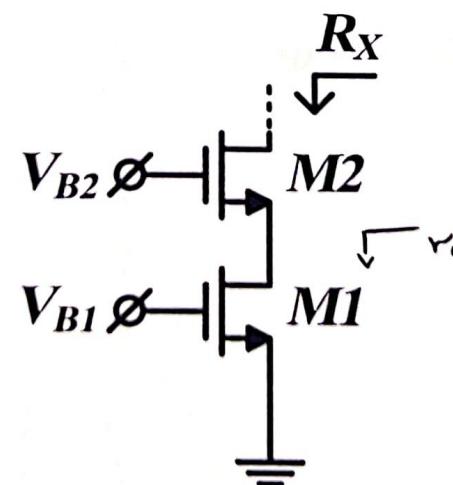
$$\therefore R_{LFD} = \bar{g}_m V_o \cdot V_o = \bar{g}_m V_o^2$$



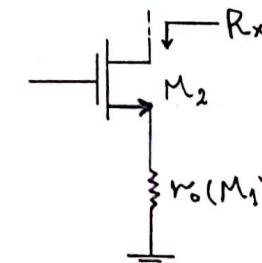2. If I have two transistor I should begin with that connected to 3rd (NMOS) and that connected to VDD (PMOS).

\*Sun, Aug, 13, 2022

- $M_1$  is special case as in AC the Gate & the Source are connected to the "Gnd" So, "Active Load"



$$R_x = R_{LFD}(M_2) = r_0 [1 + (\delta_m + \delta_{mb}) R_s]$$

$\therefore$  neglect body effect i.e.  $S_{mb} = 0$

$$\therefore R_x = r_0 [1 + \sum_m r_0(m)]$$

$$\therefore g_m \cdot w_0 \gg 1, w_0(M_2) = w_0(M_1)$$

$$\therefore R_x = r_0 [ \xi_m r_0 ]$$

$$\therefore R_X = g_m \cdot r_o^2$$

# Looking From Source

$v_{gs} = -v_x$ ,  $g_m$  and  $g_{mb}$  add, and  $g_m r_o \gg 1$

Apply KCL at S


1-  $\because$  the gate is AC ground  $\rightarrow v_{gs} = V_{BS}$   
 $\therefore (g_m + g_{mb})$

$$i_x = (g_m + g_{mb})v_x + \frac{v_x - i_x R_D}{r_o} \quad \text{equation with no unknown but } i_x \text{ & } v_x$$

$i_x$        $i_{\text{resistor}} (\text{VCCS})$        $i_{r_o}$  (Ohm's Law)

$$\therefore R_{LFS} = \frac{v_x}{i_x} = \frac{1}{g_m + g_{mb} + \frac{1}{r_o}} \left( 1 + \frac{R_D}{r_o} \right) \approx \frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right) \quad g_m v_o \gg 1$$

$g_m \gg \frac{1}{r_o}$

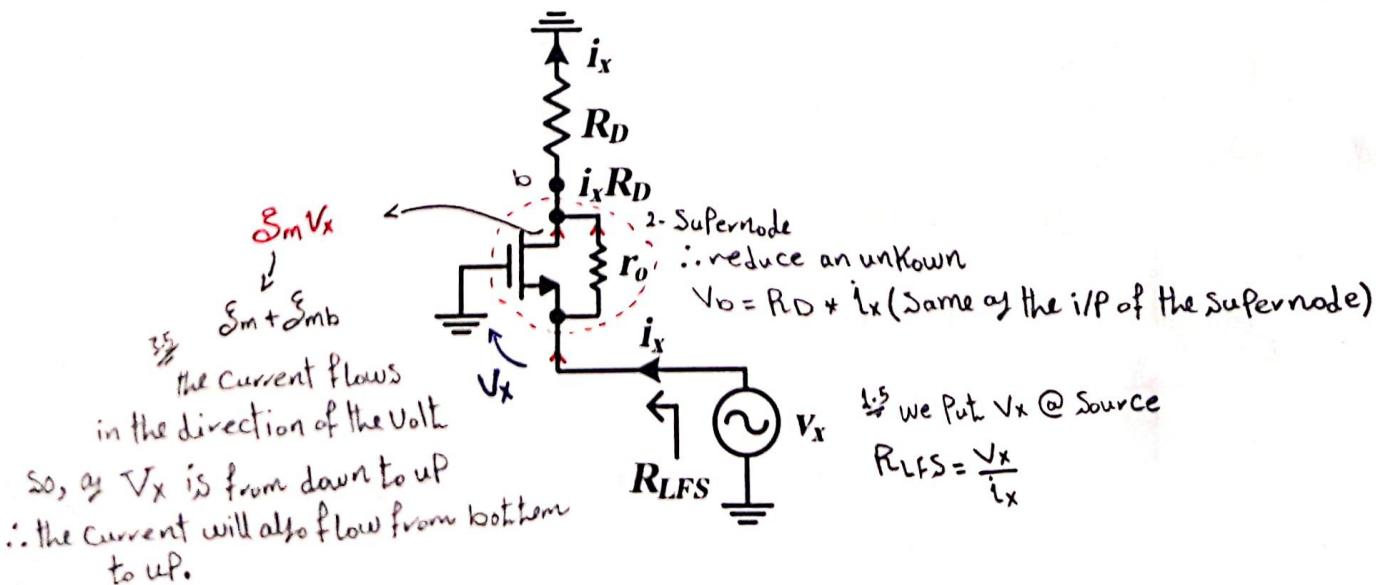


# Looking From Source

$$R_{LFS} \approx \frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right)$$

$\hat{=}$  "Diode Connected"  
Gate & Drain are AC S.C.

- Special case:  $R_D = 0 \rightarrow$  diode connected
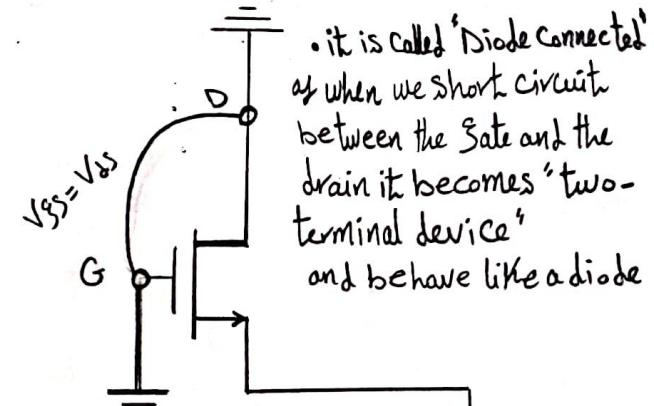
$$R_{LFS} \approx \frac{1}{g_m + g_{mb}}$$



• it is called 'Diode connected' when we short circuit between the Gate and the drain it becomes 'two-terminal device' and behave like a diode


- Source is a low impedance node (L.I.N.)

$$\hat{=}. If: R_D = 0 \rightarrow R_{LFS} = \frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right)^0$$



↳ neglecting the body effect

$$\therefore R_{LFS} = \frac{1}{g_m} \text{ which is very small. (low impedance)}$$

\* It's called 'Source Absorption'?

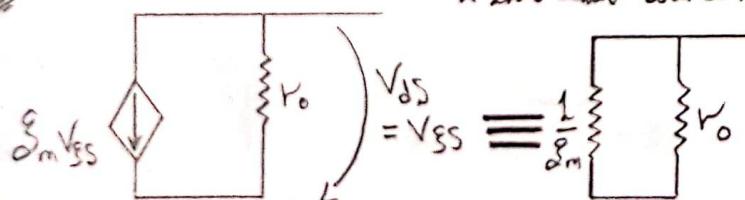

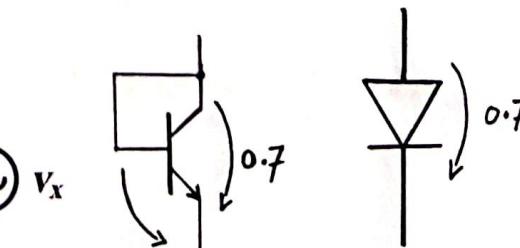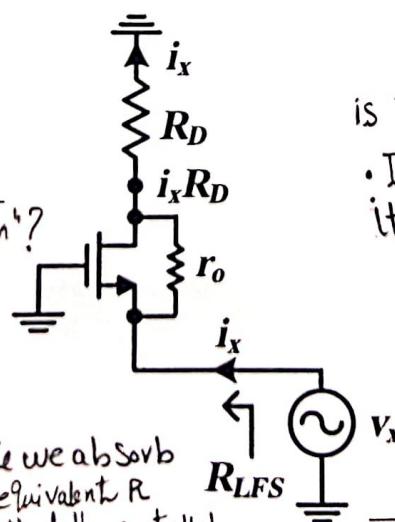- This name 'Diode connected' is inherited from the 'BJT'
- In BJT actually when it is Diode connected it will be a diode



## 06: Basic Amplifier Stages

$$R_Z = \frac{V_2}{I_Z} = \frac{V_{DS}(V_{SS})}{g_m V_{SS}} = \frac{1}{g_m} \cdot \text{Why? - As the controlling volt of the controllet Source is the same as the Voltage across the controlled Source so, it won't be Controlled Source anymore it will be a resistance.}$$

for Current Source




$$\hat{=}. But: R_{LFS} = \frac{1}{g_m + g_{mb}} \text{ doesn't contain } R_o ?$$

or from the previous approximation  $R_o \gg \frac{1}{g_m}$

$$\therefore R_o \parallel \frac{1}{g_m} = \frac{1}{g_m} \cdot \text{(but to be more accurate consider } R_o \text{ especially if } g_m \cdot R_o \text{ is small)}$$

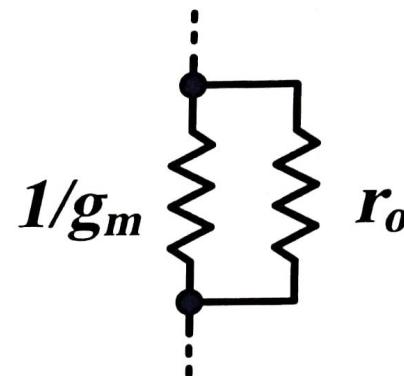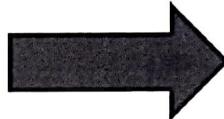
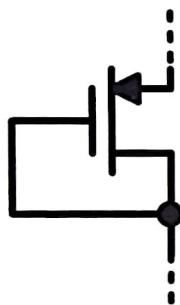
# Diode Connected (Source Absorption)

- Always in saturation ( $V_{DS} = V_{GS} > V_{OV}$ )
  - Body effect:  $g_m \rightarrow g_m + g_{mb}$  (if G is ac gnd)
- We know we are talking about large signal as we are talking about saturation but the below equivalent circuits are in small signal*
- $\therefore V_{DS} = V_{GS}, V_{GS} = V_{th} + V_{ov}$*   
 $\therefore V_{DS} > V_{ov}$



*If  $g_m \cdot r_o \ggg 1$   
 $\therefore$  this circuit is equivalent to*

$$\frac{1}{g_m}$$

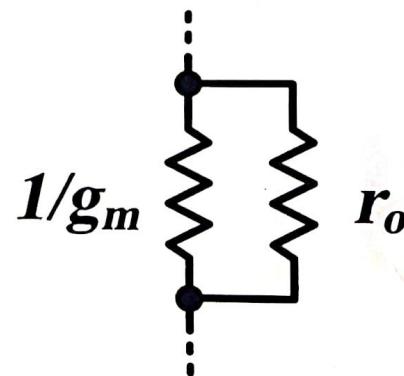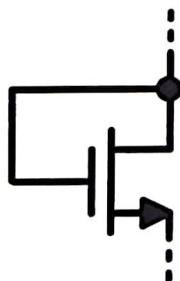

\* We can apply 'Diode connected' if the Gate & the Drain are s.c.  
 • It's not a must that both of them are connected to 'Gnd' but the condition is that they must have the same 'AC Voltage'

# Quiz


- Assume M1 and M2 have the same  $r_o$ ,  $g_m r_o \gg 1$ , and neglect body effect
- Find  $R_X$

• first I'll start with the MOSFET connected to VDD ( $M_2$ )

∴ the Source & the Gate are AC short circuit

∴ Active Load

$$\therefore R_{LFD} = r_o$$

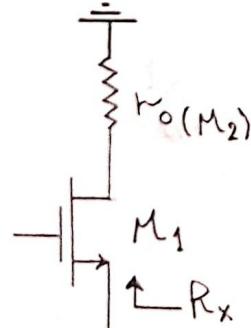


$$R_X = R_{LFS} = \frac{1}{g_m} \left[ 1 + \frac{R_D}{r_o} \right] = \frac{1}{g_m} \left[ 1 + \frac{r_o}{r_o} \right]$$

$$\therefore R_X = \frac{2}{g_m}$$

$$\star R_{LFD} \approx r_o \left[ 1 + g_m R_s \right]$$
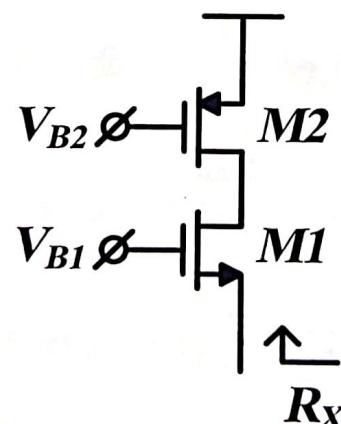
$$\star R_{LFS} \approx \frac{1}{g_m} \left[ 1 + \frac{R_D}{r_o} \right]$$



# Quiz

- Assume M1, M2, and M3 have the same  $g_m$  and  $r_o$ ,  $g_m r_o \gg 1$ , and neglect body effect

- Find  $R_X$

$$\bullet R_{LFD}(M_3) = r_o$$


$$\bullet R_{LFD}(M_2) = r_o \left[ 1 + g_m R_S \right] = g_m r_o^2$$

$$\bullet R_x = R_{LFS}(M_2) = \frac{1}{g_m} \left[ 1 + \frac{R_D}{r_o} \right]$$

$$\therefore R_x = \frac{1}{g_m} \left[ 1 + \frac{g_m \cdot r_o^2}{r_o} \right]$$

$$= \frac{1}{g_m} [g_m \cdot r_o]$$

$$\therefore R_x = r_o$$

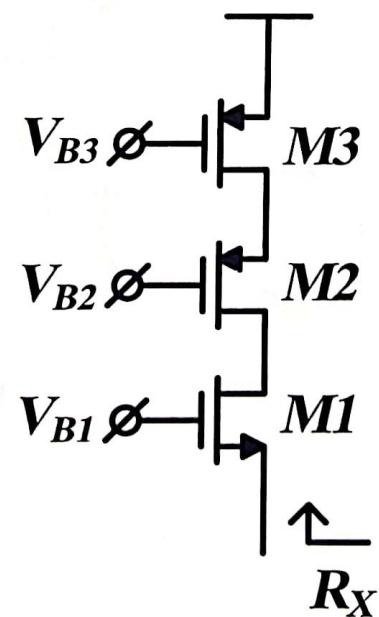

3/ You told us before that the source is low impedance node and  $R_{LFS}$  here is ' $r_o$ ' which is high impedance.

3/ Actually:  $R_{LFS} = \frac{1}{g_m} \left( 1 + \frac{R_D}{r_o} \right)$


• in normal circuit  $R_D \ll r_o$  which will result  $R_{LFS} \sim \frac{1}{g_m}$  which is low impedance.

→ But here  $R_D$  isn't a normal resistance it's ' $g_m(r_o)^2$ ' → Enormous resistance


So, the source is L.I.N except if the drain resistance is very large

Even the opposite case:

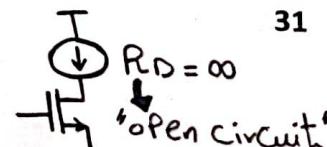• Sometimes when you look from the source you see infinity, how?!



# Rin/out Shortcuts Summary

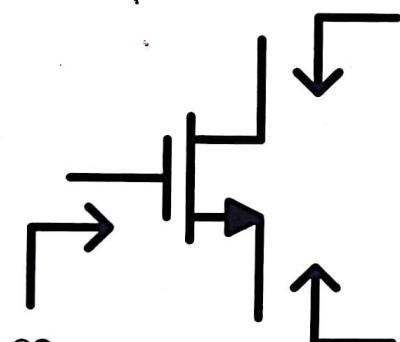

At low

frequencies **ONLY**

- as @ high frequency there will be capacitance and you should consider

\*  $\frac{1}{j\omega C}$

$$r_o[1 + (g_m + g_{mb})R_S]$$

H.I.N.

$$\frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right)$$

L.I.N.

- except
- if  $R_D$  is very large.

- Special case: "R<sub>S</sub>=0"

\* Active load

$$R_{LFID} = r_o$$

"Source off"

as  $V_{GS} = 0$   $V_{CCS}$

- Special case: "R<sub>D</sub>=0"

\* Diode connected

$$R_{LFS} = \frac{1}{g_m}$$

"Source Absorption"

as  $V_{GS} = V_{DS}$

so,  $V_{CCS} \rightarrow \frac{1}{g_m}$

# Outline

---

- Recapping previous key results
- Why amplifiers?
- Basic amplifier operation
- Basic amplifier analysis
- Rin/out shortcuts
  - Looking from drain
  - Looking from source
- GmRout method
- Basic amplifier topologies
  - Common Source (CS)
  - Common Gate (CG)
  - Common Drain (CD) – Source Follower (SF)
- Large signal behavior

# Amplifier Model

## □ Rin/out

• Thevenin resistance  
we can get by  
deactivation all the  
independent sources.

$$R_{in} = \frac{v_{in}}{i_{in}} \rightarrow \text{look from the i/P Port}$$

• look from the o/P Port  
actually it's 'Thevenin model'

## □ O.C. voltage gain (Thevenin model)

• @ open circuit  
 $i_{out} = \text{Zero}$

& Voltage drop on

$R_{out} = \text{Zero}$

so,  $v_{out,oc} = A_v v_{in}$


$$v_{out,oc} = v_{\text{Thevenin}} = A_v v_{in}$$

$$A_v = \frac{v_{out,oc}}{v_{in}} \rightarrow A_{v,oc}$$

• while solving circuit will we use  
this equation to get the gain?

- Actually No, We want to model  
the circuit @ the o/P by Norton  
model instead of thevenin.

## 06: Basic Amplifier Stages

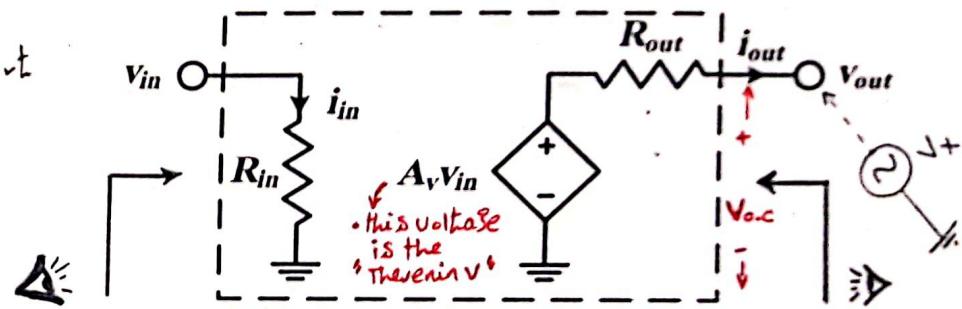

★ Voltage Amplifier  
Model

→ we called it Voltage amplifier.

• Q: we model the amplifier by input an  
input voltage "v<sub>in</sub>" and take "v<sub>out</sub>" by  
multiplying by a gain "A<sub>v</sub>".

• Actually this is not the only case as sometimes  
the input is a current, sometimes the output is  
a current, so, there are many different cases.

★ But the "Voltage Amplifier Model" is  
the most common case.

# Amplifier Model

## □ Transconductance (Norton model)

5.  $G_m$ : is the transconductance  $i_{out,sc} = i_{Norton} = G_m v_{in}$ .

for a whole circuit/whole amplifier

which can include 1, 2, 10, 20 transistors.

6.  $G_m$ : is the transconductance of a single transistor.

## □ Thevenin $\Leftrightarrow$ Norton

to relate  
both models  
to each other.

7. we compute the voltage gain ' $A_v$ '  
in two steps:

- 1- Set  $G_m$  from  $i_{out,sc} / v_{in}$
- 2-  $R_{out} \rightarrow R_{Thevenin}$

$$A_v = \frac{v_{out,oc}}{v_{in}} = G_m R_{out}$$

8. ★ the most important equation

## □ S.C. Current Gain



9. So, by computing  $G_m$  you kill  
two birds with one stone

- $\rightarrow R_{out} \rightarrow A_v$
- $\rightarrow R_{in} \rightarrow A_i$

06: Basic Amplifier Stages

$$A_i = \frac{i_{out,sc}}{i_{in}} = \frac{i_{out,sc}}{v_{in}/R_{in}} = G_m R_{in}$$

$$\frac{i_{out,sc}}{v_{in}} = G_m$$

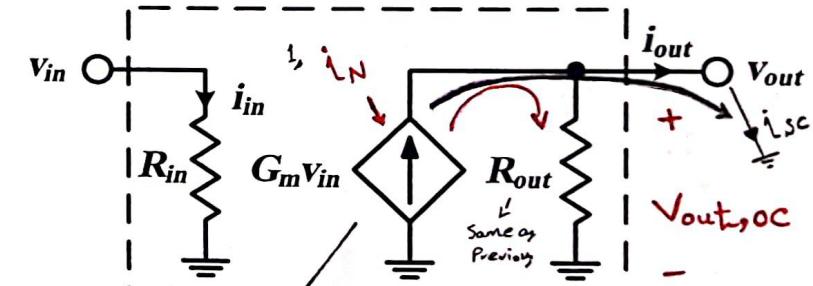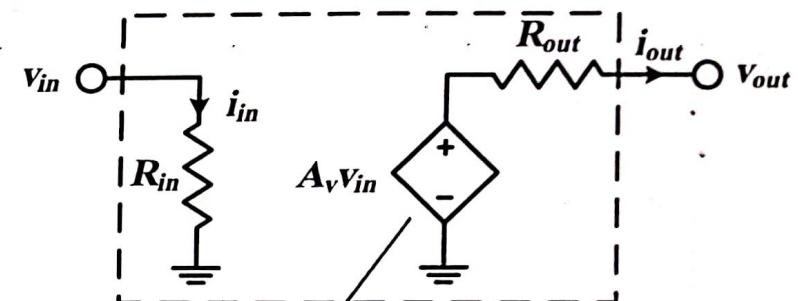

# Why GmR<sub>out</sub>?



$$R_{in} = v_{in}/i_{in}$$

$$R_{out} = v_x/i_x @ v_{in} = 0$$

$$G_m = i_{out,sc}/v_{in}$$

$$A_v = G_m R_{out}$$


$$A_i = G_m R_{in}$$

## Divide and conquer

- Rout simplified:  $v_{in} = 0$
- Gm simplified:  $v_{out} = 0$
- We already need Rin/out and Gm
- We can quickly and easily get Rin/out from the shortcuts

But you didn't tell us an important condition to consider which is  $A_v$  is the  $A_v$ , o.c. So, if we have a load every thing will change. Don't worry dude, it's very simple. Look at the Norton Model if we have a load resistance what will make you happy? - I'll be happy if the o/p is open circuit. So, put  $R_L$  inside the amplifier where Rout becomes  $R_{out}' = R_{out} // R_L$

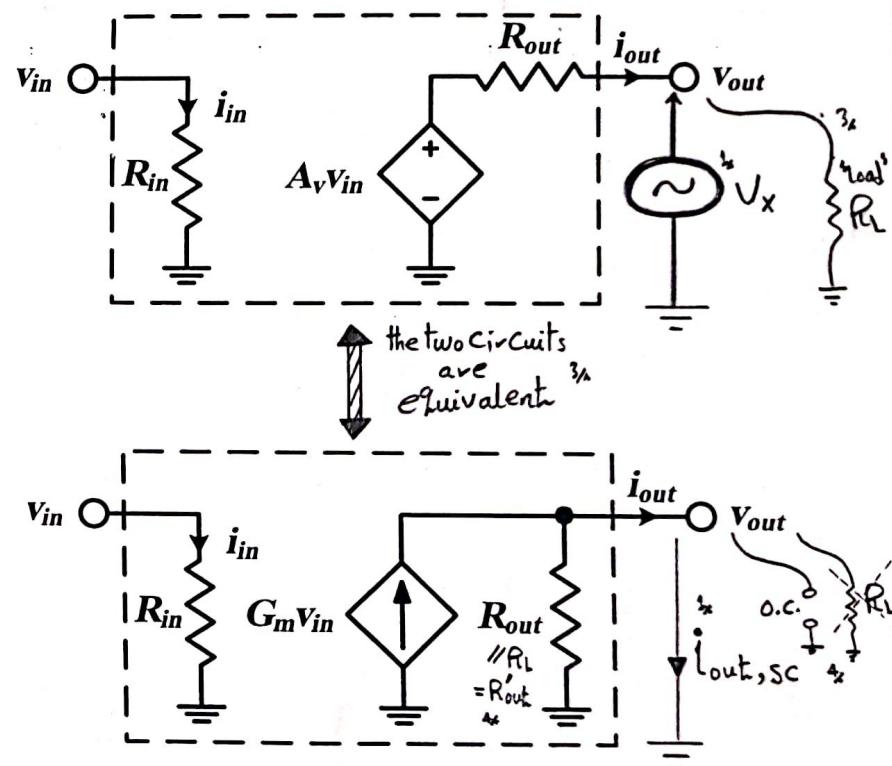$\therefore \{A_{v,oc} = G_m \cdot R_{out}'\}$  where  $R_{out}'$  is all the resistances connected to the o/p node.






# Outline

---

- Recapping previous key results
- Why amplifiers?
- Basic amplifier operation
- Basic amplifier analysis
- Rin/out shortcuts
  - Looking from drain
  - Looking from source
- GmRout method
- Basic amplifier topologies
  - Common Source (CS)
  - Common Gate (CG)
  - Common Drain (CD) – Source Follower (SF)
- Large signal behavior

# Basic Amplifier Topologies

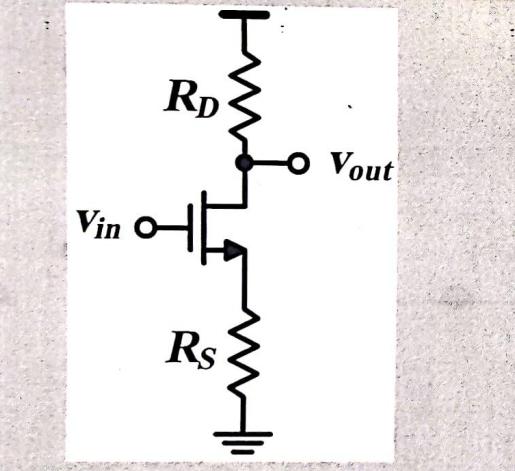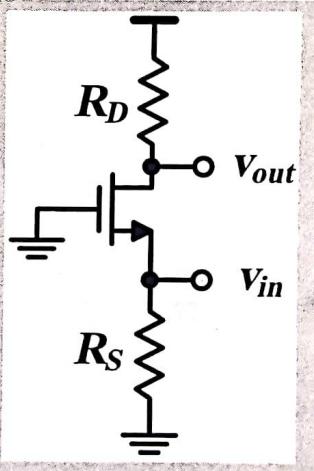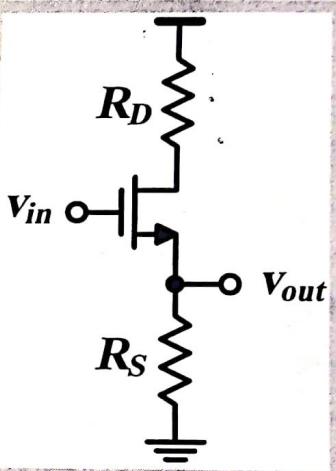Common Source (CS)	Common Gate (CG)	Common Drain (CD) Source Follower (SF)
		
Voltage & current amplifier	Voltage amplifier Current buffer	Voltage buffer Current amplifier
In	G	S
Out	D	D

$$Av = Gm R_{out}$$

# Common Source (CS)

3.  $\square$  Apply KCL at  $S$  noting that  $v_{gs} = v_{in} - (-i_{out,sc}R_S)$

$$i_{out,sc} + g_m(v_{in} + i_{out,sc}R_S) + g_{mb}(i_{out,sc}R_S) + \frac{i_{out,sc}R_S}{r_o} = 0$$

$$G_m = \frac{i_{out,sc}}{v_{in}} \xrightarrow{\text{Norton Current}} \approx \frac{-g_m}{1 + (g_m + g_{mb})R_s}$$

4/ no S.C. but we connect a test source  $V_x$  then  
 Compute  $V_x/i_x$

## 5. Some Special Cases:

□ If  $R_D$  is ac.o.c.:

□ If  $R_D \ll R_{LED}$ :

□ If  $R_D \ll R_{LED}$ :

□ If  $R_D \ll R_{LED}$ :

$$R_{out} \approx R_D \sqrt{[1 + (g_m + g_{mb})R_S]}$$


$$A_v = G_m R_{out}$$

$$A_v = -g_m r_o \quad \text{if we bias with C.S}$$


$$A_v \approx \frac{-g_m R_D}{1 + (g_m + g_{mb}) R_S}$$

$$A_v = -g_m(R_D//r_o)$$


$$\therefore A_V = -\sum_m w_m$$

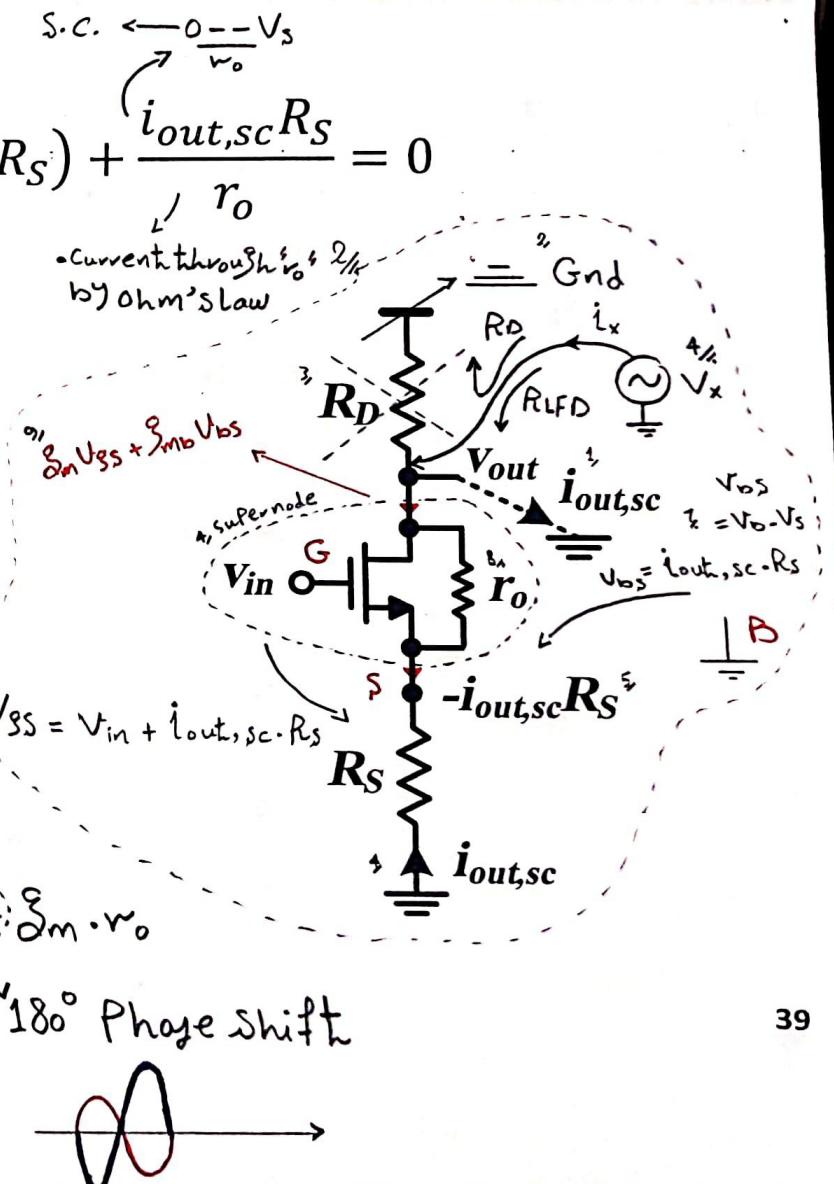

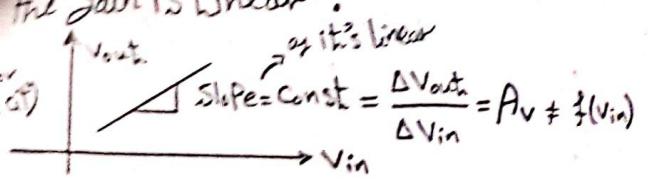3. The second special thing is that:  
the Gain is "Linear":



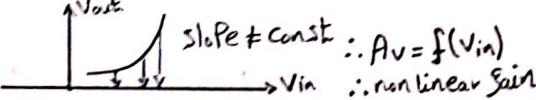3. So, to have a linear relation for the amplifier, the Gain should be constant (i.e. independent on the input).



3. You told us that  $\frac{-R_D}{R_S}$  is a linear gain, well but before ignoring the term of  $\frac{1}{g_m}$ , who said that  $\frac{1}{g_m + \text{Source Res.}}$  is not linear?

3. we assume an approximation but the gain is still not linear.

- \* Gain depends on "bias current"
- \* Bias current depends on the input voltage signal
- \* Linearization of the circuit doesn't mean it's linear
- \* there are still non-linear characteristics.

## Common Source (CS)

3. You should never make your design to depend on absolute values, for ex.

$$R_D \approx 1\text{ k}\Omega \pm 20\% \rightarrow \text{large variations}$$

$\frac{5(1K+2)}{1K+2} = 5 \therefore \text{Designing with ratios is more robust}$

This illustration is for  $\frac{5K}{1K}$  we implement  $5K$  with  $5$  series  $1K$  from the same type (for better matching)

□ If S and B are ac connected (for PMOS): (as PMOS is placed inside it's well)

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx \frac{-g_m}{1 + (g_m + g_{mb})R_s}$$


$$R_{out} \approx R_D || r_o [1 + (g_m + g_{mb})R_s]$$

$$A_v = G_m R_{out}$$

3.  $\therefore \beta_{nfb}$  at  $V_{DS} = 0$

$$\therefore G_m = \frac{-g_m}{1 + (g_m + g_{mb})R_s} (\div g_m) \rightarrow G_m = \frac{-1}{\frac{1}{g_m} + R_s}$$

$$\therefore R_{out} = R_D || r_o [1 + (g_m + g_{mb})R_s]$$

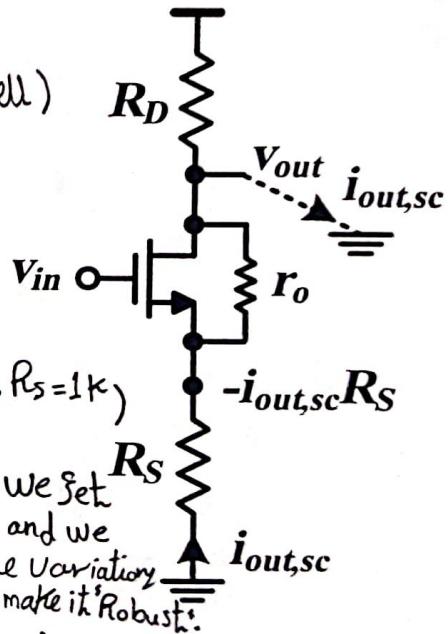

$$A_v \approx \frac{-R_D || R_{LFD}}{\frac{1}{g_m} + R_s} = -\frac{1}{\frac{1}{g_m} + \text{Source Res.}}$$

3. □ If  $R_s \gg \frac{1}{g_m}$  &  $R_D \ll R_{LFD}$ :  $A_v \approx \frac{-R_D}{R_s} \rightarrow$  Linear gain! (for ex. if  $R_D = 5K$ ,  $R_s = 1K$ )  $\therefore A_v \approx -5$

3. □  $R_s$  reduces  $G_m \rightarrow$  Source degeneration  
▪ But improves linearity

3. what's special in this eq. is that we set the gain as a ratio of two resistors, and we know that in analog design as a result of the variation in the IC, designing the design as a ratio of parameters make it 'robust'.

3. We can use the assumption of S and B are ac connected for:

- PMOS • NMOS (triple well)

3. In the simulation: in the small signal parameters  $\beta_{nfb}$  will have a value, but does this value have a meaning or it's meaningless it depends on the connection of the source & the body.

11/ Designing by a ratio guarantees that the gain is linear across the variations.

• Variations  $1K \pm 20\%$  \* Variation vs. Mismatch • If in the layout mean that we can't control the absolute value of the component (we can't know accurately the absolute values) but they will still be the same, will they or some variations be exactly the same? - of course No

• There will be a small error (called the mismatch) this is because mismatch is a result that the machines used to manufacture the ICs have their noise and tolerances. Actually in ICs the devices are very close to each other (dimensions by  $\mu m$ )

• Mismatch can be better than 1% ( $< 1\%$ ) so the error will be  $< 1\%$  not  $> 20\%$  of  $(1K \pm 20\%)$

## 12/ $R_s$ : Degeneration Resistor


• we called this amplifier "Degenerated Common Source"

→  $R_s$  reduces  $G_m$  so, reduces the gain (so, why we put it?)

→ we use it as it "improves the linearity"

@ the ultimate case it makes the gain ratio of resistors  $\frac{R_D}{R_s}$  (linear gain)

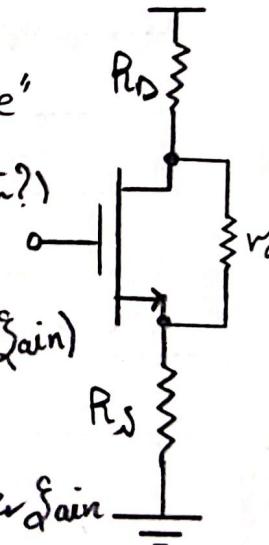and even if we don't neglect  $(\frac{1}{g_m})$  it still reduces the effect of the variations occur in  $(g_m)$  over the amplifier gain



\* trade-off Gain Linearity and this trade-off is always there in the feedback systems and  $R_s$  is doing some sort of feedback we can have a look later when we study feedback.

\* In this ideal case: Input Impedance =  $\infty$  so, Current Gain  $A_i = -G_m R_{in} = 0$

\* Notice that when we calculated "Rout" we took into consideration all the resistances connected to the output node. It's a trivial result as it absorbs no current.

Some technique, write the analysis  
on the schematic then single KCL

Divide & Conquer

$$A_v = G_m R_{out}$$

output  $\rightarrow$  S.C.      input  $\rightarrow$  S.C.

# Common Gate (CG)

3.  Apply KCL at D noting that  $v_{gs} = v_{bs} = 0 - v_{in}$

When we calculate  $R_{out}$   $i_{out,sc} + (g_m + g_{mb})(-v_{in}) - \frac{v_{in}}{r_o} = 0$

$$R_{out} = \frac{V_x}{i_x} \quad |_{V_{in}=0}$$

$\therefore$  we omit  $R_s$  Deactivation to the input source  
so, when looking we won't see anything but  $r_o$

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx g_m + g_{mb}$$

$\text{R}_{out} = \text{Parallel resistances} \quad R_{out} \approx R_D || r_o \quad (\text{why?})$

1. @ the output node 1-up:  $R_D$ , 2-down: supposed to be RLFD like "CS" but instead we are seeing " $r_o$ " why?

8.  If  $R_D$  is ac o.c.:  $A_v = (g_m + g_{mb})r_o$  ★ In this case:  
"S<sub>mb</sub>" gives bigger gain than the "intrinsic gain"


9.  If  $R_D \ll r_o$ :  $A_v \approx (g_m + g_{mb})R_D$

10.  If S and B are ac connected:  $(g_m + g_{mb}) \rightarrow g_m$

11.  Note that  $A_i = G_m R_{in} \ll 1$  (Current Buffer)

06: Basic Amplifier Stages

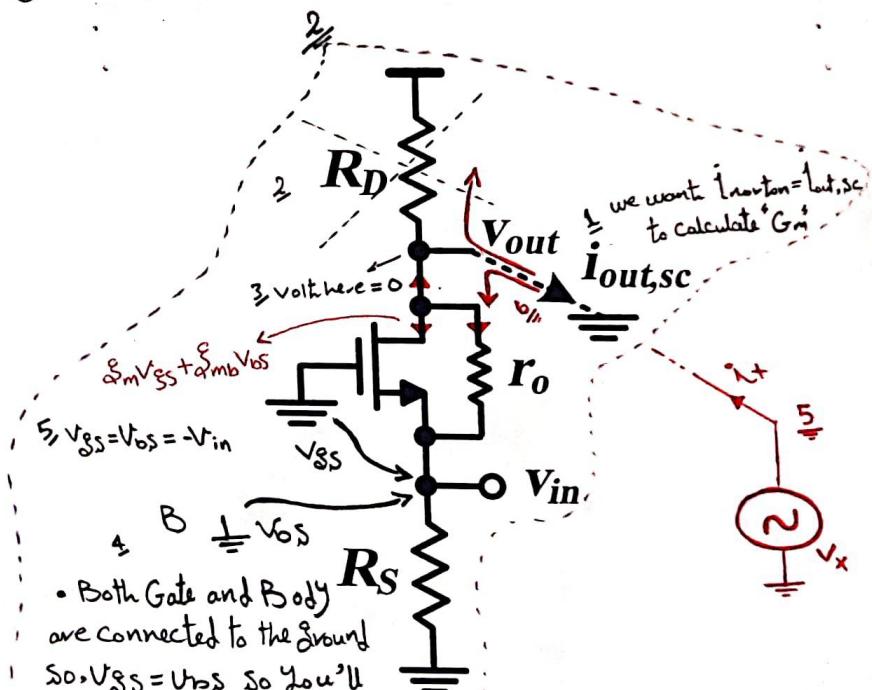9. Note that the Gain is Positive i.e. no Phase inversion like CS.



• Both Gate and Body are connected to the Ground  
so  $V_{GS} = V_{BS} = -V_{in}$  So you'll always see  $G_m$  and  $G_{mb}$  are added together in the equations  
(unlike CS amplifier we saw  $(G_m + G_{mb})$  in the denominator but in the nominator only  $G_m$ )

★ One of the important notes is that the Common Gate (CG) is voltage amplifier but "Current Buffer", Why?


Sense

- We have the input @ the source and the output @ the drain
- and we know that the current @ the gate = zero and the current of the source is roughly equal to that of the drain so, it's rational to say that it won't amplify the current

★ the currents flowing through both the source & the drain are the same.

★ even Practically (the gain < 1)

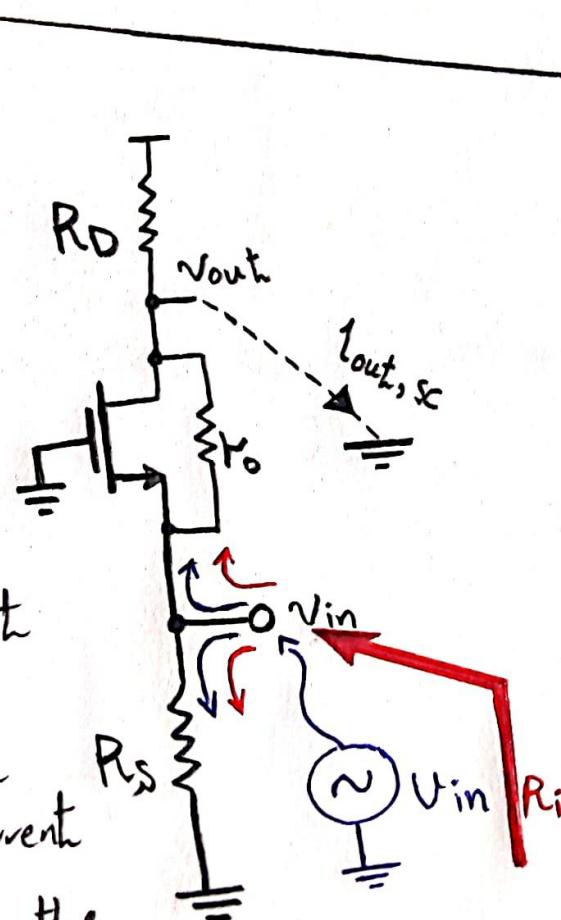- As part of the current coming from the input source will flow through "R<sub>S</sub>" and the rest flow through source then drain.



Equations

• Short circuit current gain

$$A_i = g_m \cdot R_{in}$$

-if there is no body effect (for simplicity)  
 $= g_m$

$$R_{in} = R_S \parallel R_{LFS}$$

• Assume  $R_D \ll r_o$

$$\therefore R_{LFS} = \frac{1}{g_m}$$

the biggest value for this expression occurs when "R<sub>S</sub> = ∞"

So, when  $R_S = \infty$

$$A_i = g_m * \frac{1}{g_m} = 1$$

\* So with R<sub>S</sub> there

$A_i < 1$  (intuition results verified)  
successfully #

% Same as Previous  
Gm Rout

# Common Drain (CD) – Source Follower

- Apply KCL at D

6

$$+ i_{out,sc} - g_m v_{in} + \frac{- (o - i_{out,sc} R_D)}{r_o} = 0$$


leaving the node

entering the node

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx \frac{g_m}{1 + R_D/r_o}$$

$\therefore G_m \approx g_m$  same as "CG amplifier"

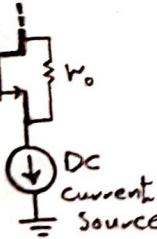$\therefore$  the biggest value for  $R_{out}$  when  $R_S = 0.C.$  which means when replaced by DC current source



$$R_{out} \approx R_S \parallel \frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right)$$

$$A_v = G_m R_{out} \rightarrow R_{LFS}$$

- If  $R_S \gg R_{LFS}$ :  $A_v \approx \frac{g_m}{g_m + g_{mb}} < 1$  → and this is the largest gain

- If S and B are ac connected (for PMOS): (no body) effect

$$A_v \approx 1 \text{ (Voltage buffer)}$$

$\frac{1}{2}$  Practically  $< 1$   
of the current source omitted by S.C.  
 $\therefore R_S$  will be omitted by S.C.

$\frac{1}{2}$  Also another advantage is that CD Provides "Current Gain"  
→ Ideally absorbs zero current as  $R_{in} \uparrow \uparrow$  and provides current

06: Basic Amplifier Stages 13 So, What is the benefit of the CD amplifier?

- It isolates the output from the output.

Previous Stage Input Impedance  
There is no "loading effect" on the previous stage as it'll have infinite impedance

$\rightarrow$  The output will see low output impedance  
 $\rightarrow$  low output impedance  
 $\rightarrow$  Buffer  $\rightarrow R_{in} \uparrow \uparrow$   
 $\rightarrow$   $R_{out} \downarrow \downarrow$

# Summary of Basic Topologies

$$g_m \cdot r_o \gg 1$$

$$r_o > \frac{1}{g_m}$$

anything of  
no order is  
high impedance

anything of  
1/2 order is  
low impedance


- \* for CS if we replace  $R_D$  with DC current source will the amplifier operate well?
- Yes and the gain will increase as  $A_{vout} = (R_D || r_o) [1 + (g_m + g_{mb}) R_S]$
- \* What about replacing  $R_S$ ?
- The answer is no it will not work.

why? -  $\frac{1}{g_m}$

$$\frac{1}{1 + (g_m + g_{mb}) R_S}$$

$$\therefore G_m = 0$$

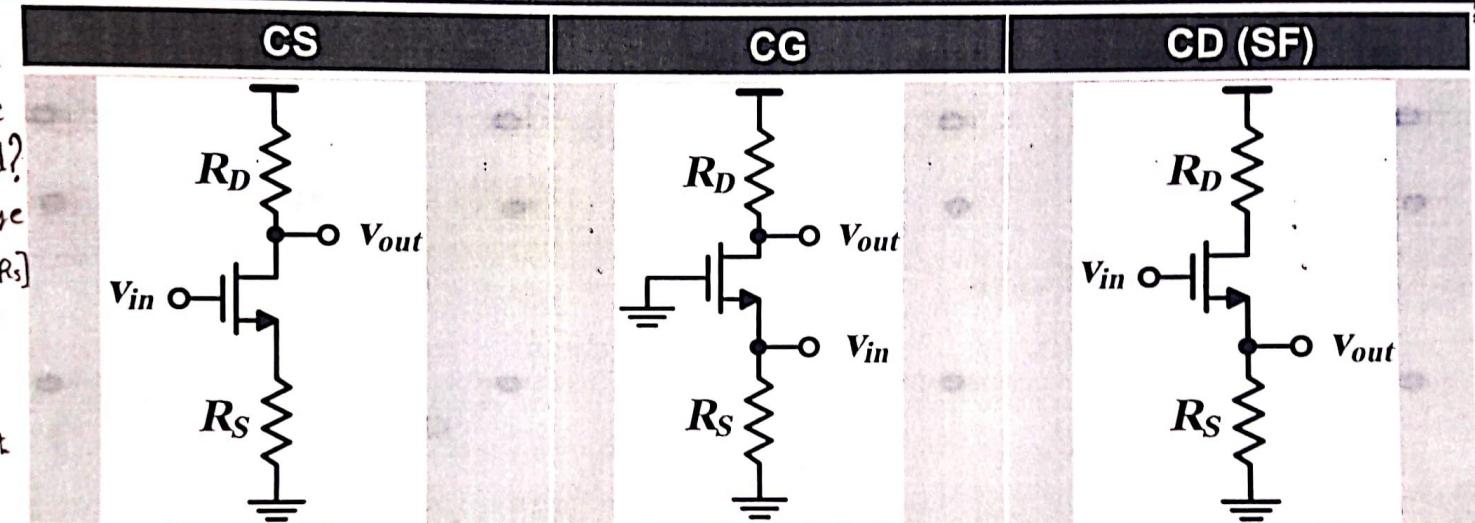
- بوتات الأمبليفياتر  
الحال واحد غيره (ع)
- \* We'll face this case later @ Diff. Amplifier.



Rin	$\infty$	large Rin	$\infty$
Rout	$R_D    r_o [1 + (g_m + g_{mb}) R_S]$	• Also large Rout as ( $R_{LFD}$ )	$R_D    r_o$
Gm	$\frac{-g_m}{1 + (g_m + g_{mb}) R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$

Also, it's better in the common drain as previously said is to replace  $R_S$  with DC current source for not distributing the current between the  $R_S$  and the load resistance or the next stage

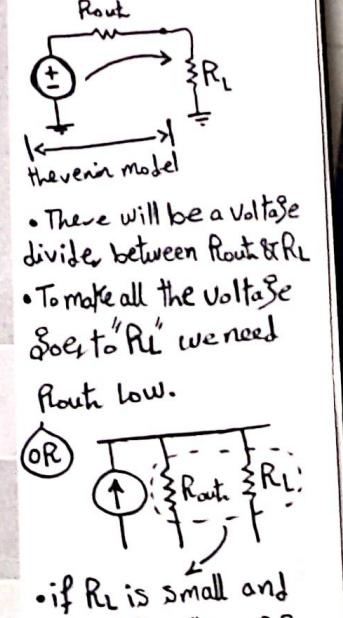$\frac{1}{g_m} \cdot R_D \cdot r_o \gg 1$   
so, it's rational not to add  $R_D$  and replace it with S.C.  
• Will it operate then? - Yes, common drain means that the drain is grounded @ the  $g_m$  model



$\frac{IN \rightarrow Source}{OUT \rightarrow Drain}$  } Common Source

No resistance @ the drain and even in the previous analysis.

\* In ICs we rarely use resistors but loads are implemented using transistors (every thing is expressed using transistors) and then we can replace that transistor with equivalent R.

## Quiz

- The circuit below shows a CS amplifier With diode-connected load
- Find the gain using  $GmR_{out}$  (ignore body effect and CLM).
  - Express the gain in terms of  $(W/L)_1$  and  $(W/L)_2$ .
- This is a "linear" CS amplifier.

\*  $G_m = \frac{-g_m}{1 + g_m R_s}$  (Should be memorized)

$\therefore G_m = -g_{m_1}$  as  $M_1$  is the Mos responsible of the amplification process or the transconductance (convert  $V_{in}$  to  $i_{out}$ )

$$R_{out} = \frac{1}{g_{m_2}} \parallel r_o$$

as source off so, there is only  $r_o$

- neglect  $r_o$

$$\therefore R_{out} = \frac{1}{g_{m_2}} \rightarrow \therefore A_v = -\frac{g_{m_1}}{g_{m_2}}$$

06: Basic Amplifier Stages

not very interesting until expressing  $g_m$  with an equation

But which one? (3 expressions) the one with  $W/L$  & current

we told me to express

$$\rightarrow R_D \approx \frac{1}{g_{m_2}}$$

to be distinguished of  $g_{m_1}$  as both are different as they have different sizes

$$\therefore A_v = -\frac{g_{m_1}}{g_{m_2}} = \frac{\sqrt{M_1 C_{ox} (\frac{W}{L})_1 2f_D}}{\sqrt{M_2 C_{ox} (\frac{W}{L})_2 2f_D}} = \sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

\* Interesting as the gain is expressed as a ratio


→ Good design depends on ratio not absolute.

\* Interesting as its ratio of sizing  $\neq f(V_{in})$  i.e. "linear"

→ There were many approximations  
- we neglect  $r_o$  and body effect for  $M_1$

\* Actually you won't have a great gain as source floating

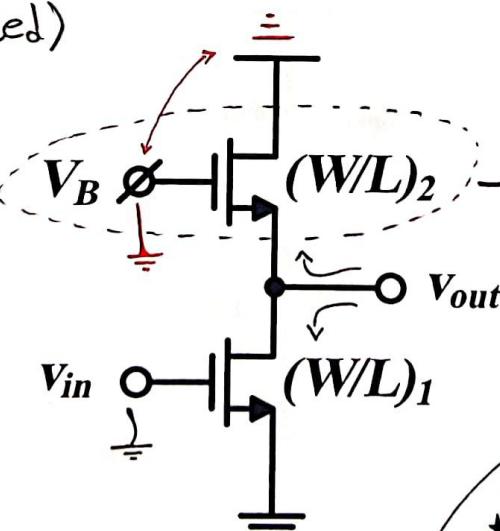$\frac{g_{m_1}}{g_{m_2}}$  so, it's trade-off



there is a special property  
the current in the whole branch  
is the same (through  $M_1$  &  $M_2$ )

# Quiz

★ If you notice this amplifier is like "CMOS Inverter" in digital so, it's called "inverter amp." and it's the same circuit as the CMOS inverter and sometimes it's called "Complementary Common Source amp." and its disadvantage is that it has (very) poor power supply rejection, will be discussed later.

- The circuit below shows a complementary CS amplifier (inverter amp).
- Find the gain using  $GmR_{out}$ .

• Here this example is a bit complex as there are two amplifiers not one  
→ The input enters both  $M_1$  &  $M_2$


\* First solution (which will enable us to make use of the shortcut is the Superposition

$$\begin{aligned} \textcircled{1} \quad \frac{V_{out}}{V_{in}} &= G_m R_{out} \\ &= -\delta m_1 (r_{o1} \parallel r_{o2}) \end{aligned}$$

$$\begin{aligned} \textcircled{2} \quad \frac{V_{out}}{V_{in}} &= -\delta m_2 (r_{o1} \parallel r_{o2}) \\ \therefore \text{By sum } \textcircled{1} \& \textcircled{2} \end{aligned}$$

$$\therefore \frac{V_{out}}{V_{in}} = -(\delta m_1 + \delta m_2) (r_{o1} \parallel r_{o2})$$

06: Basic Amplifier Stages

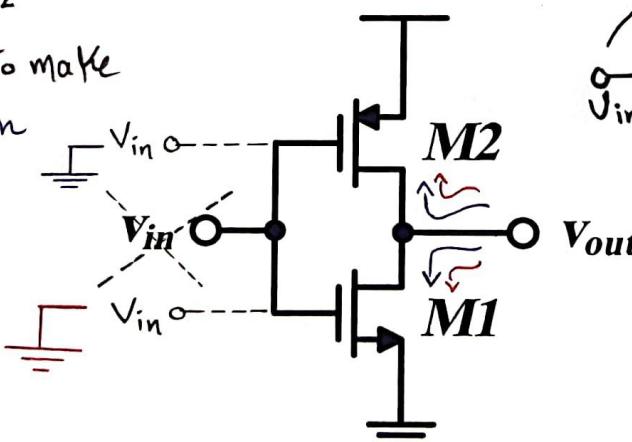

★ Notice that:

This amplifier gives us an important property which is increasing "Gm" instead of  $G_m$  45 of one transistor it gives the  $G_m$  of two transistors so, it's (Energy) Efficient → large  $G_m$  + low bias current

★ Another solution is to calculate " $G_m$ " by definition

$$G_m = \frac{i_{out,sc}}{V_{in}}$$

"Simply the MOS model is a current source & a resistance"

\* APPLY KCL @ X

$i_{out,sc} = \delta m_2 V_{in} + \delta m_1 V_{in} + i_{out,sc}$

the two resistances are omitted as they have two grounds @ each terminal

$\therefore i_{out,sc} = -(\delta m_1 + \delta m_2)$

\*  $V_{in}$

$\therefore G_m = \frac{i_{out,sc}}{V_{in}} = -(\delta m_1 + \delta m_2)$

$$\therefore A_v = G_m R_{out} = -(\delta m_1 + \delta m_2) (r_{o1} \parallel r_{o2})$$

# Outline

---

- Recapping previous key results
- Why amplifiers?
- Basic amplifier operation
- Basic amplifier analysis
- Rin/out shortcuts
  - Looking from drain
  - Looking from source
- GmRout method
- Basic amplifier topologies
  - Common Source (CS)
  - Common Gate (CG)
  - Common Drain (CD) – Source Follower (SF)
- Large signal behavior

# CS Amplifier Example

$$\frac{1}{2} \cdot A_v = G_m R_{out}$$


$$\approx -g_m (R_D \parallel r_o)$$

no degeneration

$$\approx -g_m R_D \rightarrow R_D \ll r_o$$




Important note to remember is that the signal is superimposed on a DC volt.

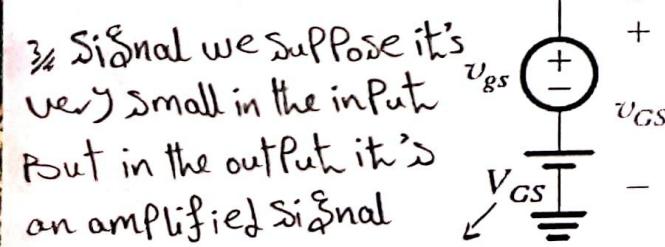In input:  $v_{GS}$ , In output:  $v_{DS}$



So, How we say that the small signal approx. is still valid while we have large signal @ the output?  
06: Basic Amplifier Stages

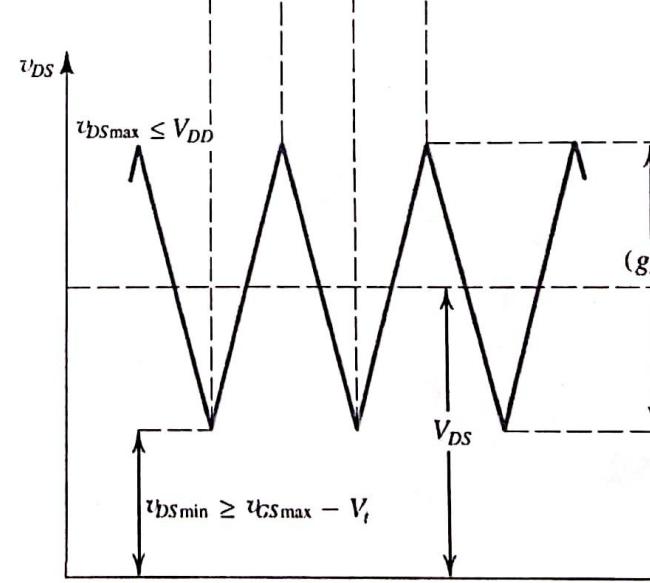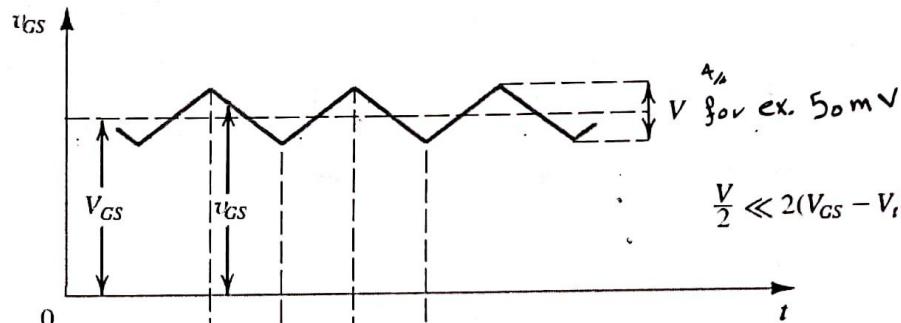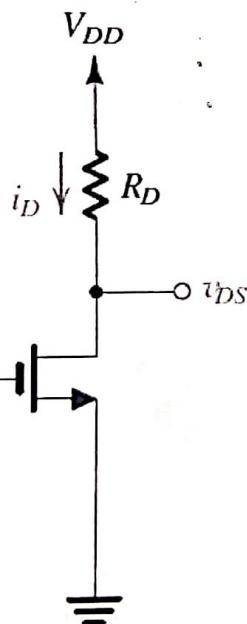If we consider 50 mV of small signal we can't consider 500 mV (0.5 V) of small signal.




$$\text{for ex. } |A_v| = g_m R_D = 10$$

We were interested to apply the small signal  $v_{GS}$  approx. on the ch. of the input side but ideally the output side has no effect on the current and the MOS.


The Answer is that we actually are interested [Sedra/Smith, 2015] with the small signal @ the input not the input of ideally the current of the transistor doesn't depend on "v<sub>DS</sub>" it's v<sub>GCS</sub> (current source means that its current doesn't depend on the applied voltage) so it's supposed that v<sub>DS</sub> has no effect on the transistor.

7. Does this mean that the output can change freely and amplifier won't be affected?  
 - Of course No, There are limits, we'll permit large signal variation @ the output with limits.

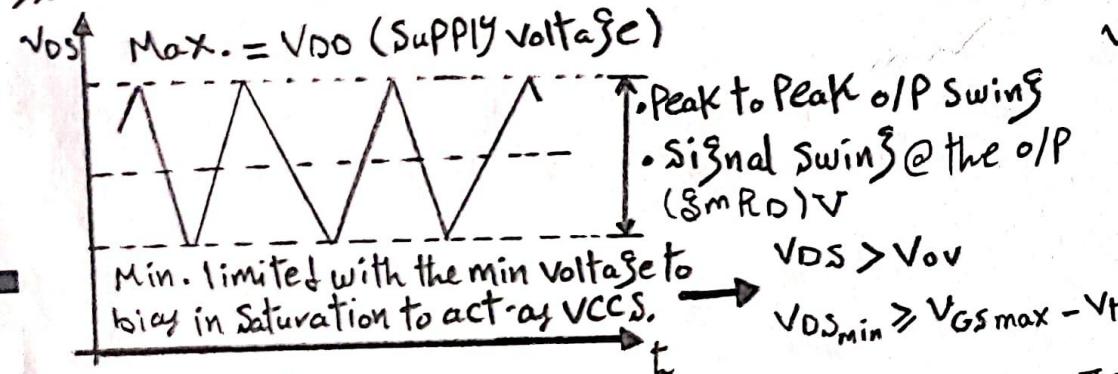8. What are the limitations of the output swing (the larger (Max.) and Min. Values for the output)?


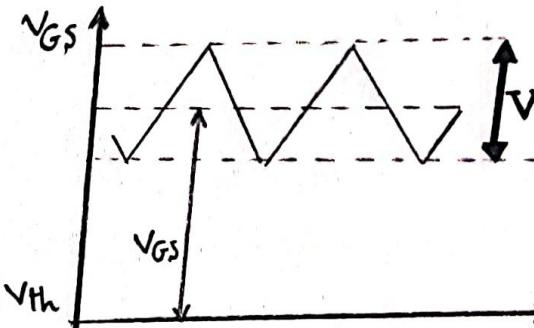
$$\therefore \text{Max. Signal Swing} = V_{DD} - V_{ov}$$



- We assume small signal @ the i/p what are the boundaries?
  - If for ex. 50mV how to know it's small or large signal?
- (1) By analysis: Substitute in the equation  
 (i.e. Solve the amplifiers with the square law (non-linear model))



Then it will result that the gain is non linear function then search for the condition at which this non-linear function can result linear gain by neglecting the non-linear part and this analysis can be found in (Sedra-Smith).

\* The result in this case is the amplitude  $\frac{V}{2} \ll 2(V_{GS} - V_t)$ ,  $\left\{ \frac{V}{2} \ll 2V_{ov} \right.$

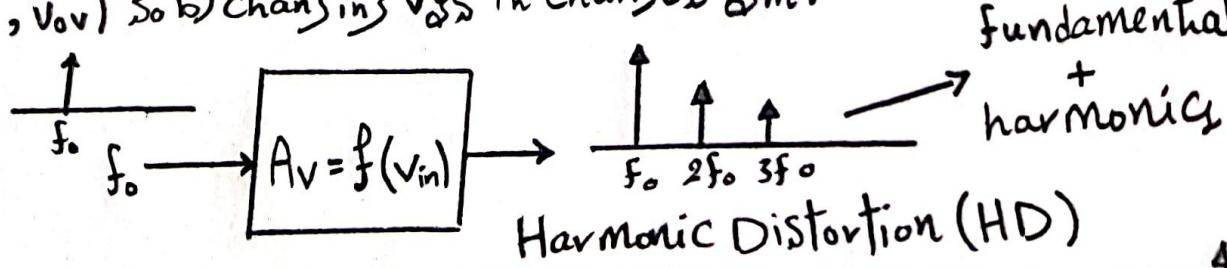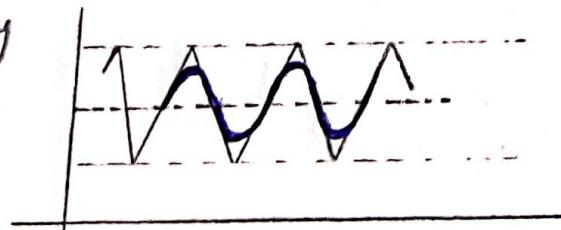(2) By intuition:  $\Delta V_{GS} \ll V_{ov}$  rough estimation

\* We said that increasing 'R\_s' linearize the amplifier but why? - as not all the  $V_{in}$  will be translated as  $V_{GS}$  but some of  $V_{in}$  will be a voltage drop on 'R\_s' so, the part be  $V_{GS}$  will result the non linearity and the other part will go to  $R_s$ , and by increasing  $R_s$ , smaller part will go to  $V_{GS}$ .  
 \* This non linearity is a result that  $\delta m$  is a function of  $V_{in}$  ( $f(V_{in})$ )  
 Or  $\delta m = f(V_{in}, V_{ov})$  so by changing  $V_{GS}$  it changes  $\delta m$ .

\* This non linearity is interpreted as "Distortion".



# CS Large Signal Behavior

"other Perspective from Razavi Book"

- Gain is non-linear:

$$\frac{A_v}{\text{slope}} = f(V_{in}) = g_m \cdot R_D$$

$$g_m = f(V_{in})$$

- For linear gain,  $A_v$  should NOT be  $f(V_{in})$


- $A_v$  and  $g_m$  are max at edge of triode

- But they are highly non-linear
- And the available signal swing vanishes

During the simulation you'll see a bit different results?  
- As we ignored " $V_o$ "


$A_v = -g_m (R_D || V_o)$

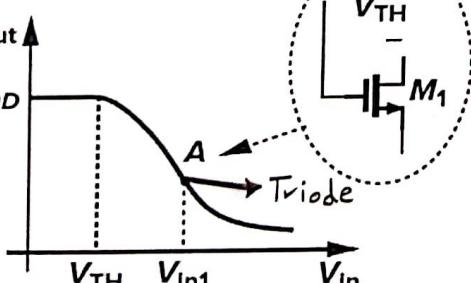$\therefore V_o \downarrow \rightarrow r_o \uparrow$   
 $\therefore r_o$  is decreasing  
 $\therefore$  the slope is increasing



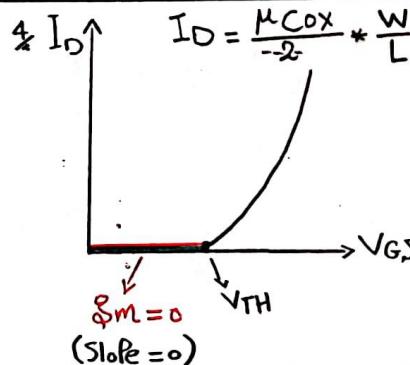
## (06: Basic Amplifier Stages

While going through the curve approaching the triode region  $\rightarrow r_o$  is decreasing of Saturation then it'll compress until it reaches the largest possible value ( $V_{DD}$ ) and the reason for that is by increasing  $V_{in}$  then  $I_D$  increase  $\therefore$  @ the edge of saturation  $r_o$  is small while  $V_{out} = \frac{V_{DD}}{R_D}$  is decreasing and ultimately the Min. value for  $V_{out} = 0$  @ going deeper into triode  $\rightarrow$  slope  $\uparrow \uparrow \rightarrow r_o \downarrow \downarrow \rightarrow A_v \downarrow \downarrow$  which you'll set the lowest current by ohm's law ( $V_{DD}/R_D$ ).]




$\frac{dI_D}{dV_{GS}} = \frac{\mu_Cox * W}{L} V_{GS}^2 \rightarrow \frac{dgm}{dV_{GS}} = \mu_Cox \frac{W}{L} V_{GS}$

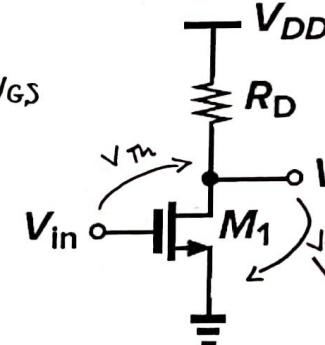linear  $V_{GS} \uparrow \therefore g_m \uparrow$  until reaching Point 'A' in  $(g_m - V_{in})$  curve as @ Point 'A' you'll leave saturation and the above equation won't be valid.



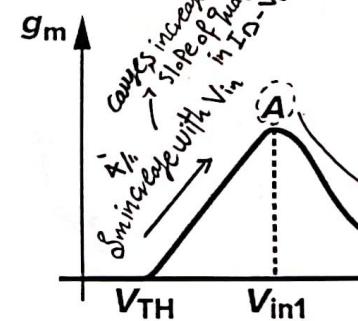You can know the edge of saturation by two ways:  
a) This voltage ' $V_{DS} = V_{ov}$ '  
b) or saying that there's channel @ the drain i.e.  $V_{GD} = V_{in}$



Till  $V_{in}$  the current almost equals zero then it'll increase "Quadratically" until it leaves the region [Razavi, 2017]  
Drawing the Gate connection taller than the Drain meaning that its voltage is higher.  
@ the edge of saturation  $\therefore$  Largest  $A_v$   
 $\therefore$  But  $V_{out} = V_{ov}$   
 $\therefore$  No available signal swing

\* The negative swing will set the Mos out of saturation.

# Output Signal Swing

$$V_{out,max} = V_{DD} - V_{ov2}$$


$$V_{out,min} = V_{ov1} = V_{in,max} - V_{TH}$$

□ Output swing  $\approx V_{DD} - 2V_{ov}$  If  $V_{ov1} = V_{ov2}$

∴ The available range:


- The chair height:  $V_{ov}$  for the MOS beneath  $V_{ov_1}$
- The ceiling: is not  $V_{DD}$ , why?
- As we have above a MOS we want also to operate @ the saturation (current source) so, it's need to apply bias voltage on it  $V_{ov_2}$  (lamp)
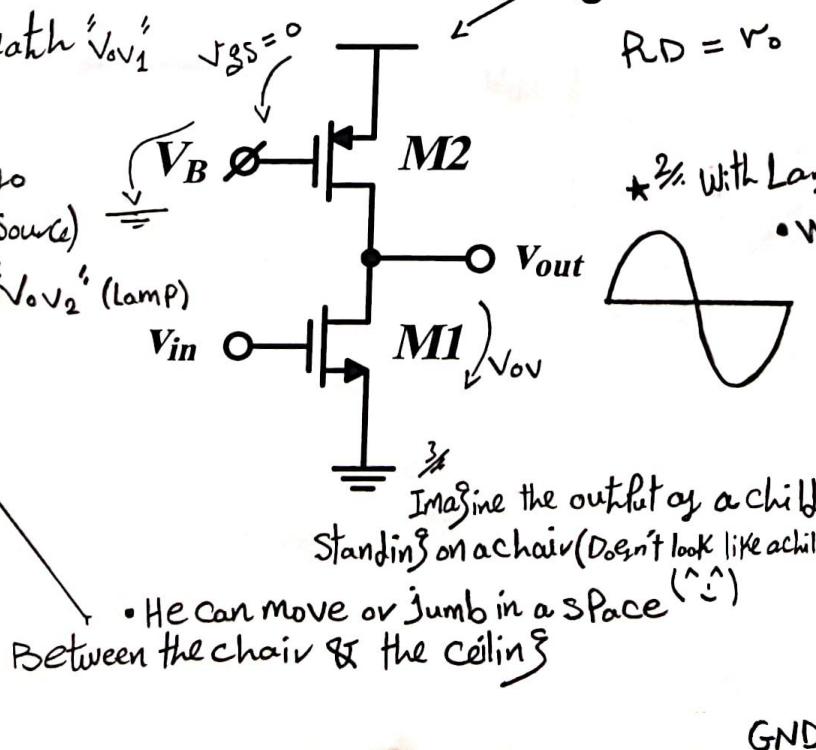
$$\therefore \text{The ceiling} = V_{DD} - V_{ov_2}$$



\* 1/4. Same as the CS Amplifier  
But we replace "R\_D" with active load.  
 $R_D = r_o$

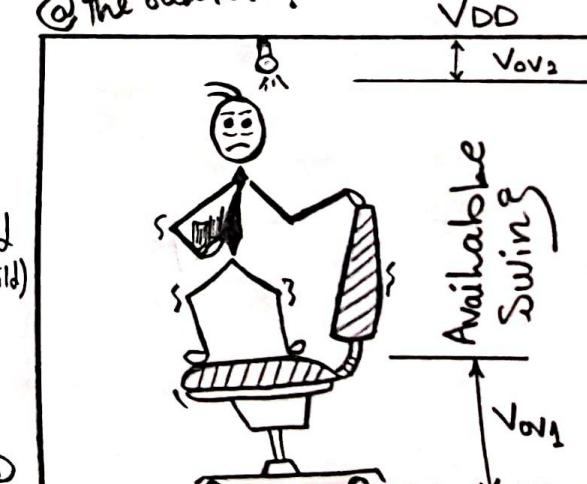\* 2/4. With Large Signal Perspective  
• What's the available signal swing  
@ the output?



# CD Large Signal Behavior

## □ Why Source Follower?

- Buffer
- Level-shifter

∴ In the Large Signal 'CD' has another use:

- used in Level Shifting


→ You told us that CD is a source follower and  $V_{out} = V_{in}$ ?  
- It's right in small signal not in large signal

\* In Large Signal: APPLY KVL to get  $V_{out}$



$$\therefore V_{out} = V_{in} - V_{GS}$$

shift (Down Shifting)

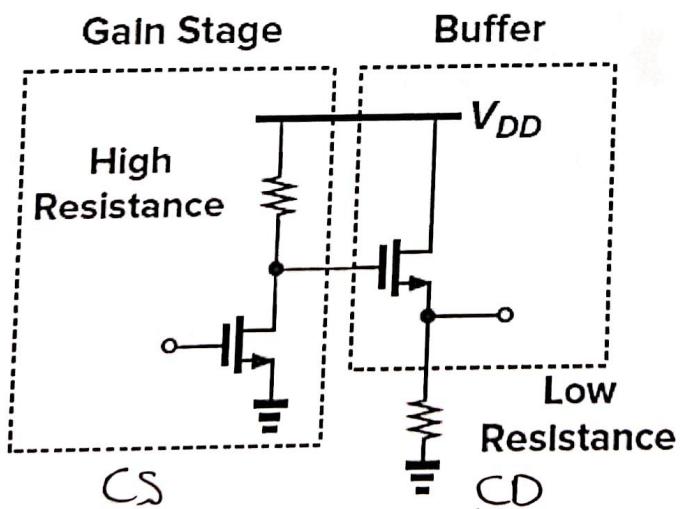
as a result that  $V_{GS}$  is changing (unless  $I_D = \text{Const.}$ )  
this shifter won't be ideal i.e. some sort of error.



∴ act as a buffer  
with the Gain Stage

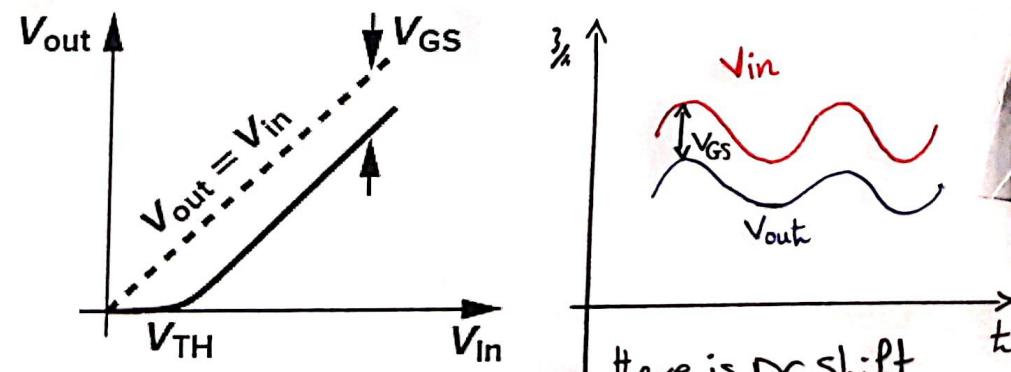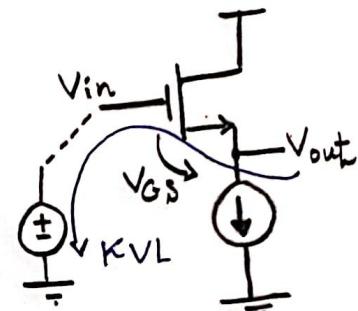

there is DC shift  
 $= V_{GS}$

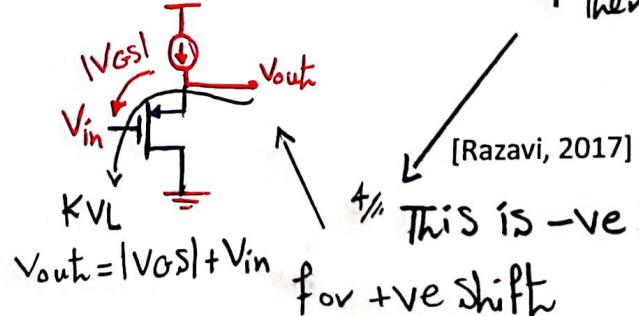

∴ This is -ve shifting  
for +ve shift

# Thank you!


Dr. Hesham Omran's Lecture  
Fady Sabry Negm's notes

# Quiz (1): lecture (6)

\* Quiz on:  
"hooking from Drain"

- Assume  $M_1$  and  $M_2$  have the same  $\beta_m$  and  $r_o$ ,  $\beta_m r_o \gg 1$ , and neglect body effect
- Find  $R_x$

Sol.

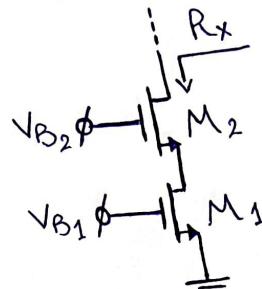

• for  $M_2$ :

$$\rightarrow R_{LFD2} = r_o [1 + (\beta_m + \beta_{mb}) R_{S2}]$$

$$R_{S2} = R_{LFD1}$$


• for  $M_1$ :

$\because R_S = 0, R_G = 0$  (i.e. AC connected to the Gnd.)

$$\therefore R_{LFD1} = r_{o1} = r_o$$

$$\therefore R_{LFD2} = r_{o2} [1 + (\beta_m + \beta_{mb}) r_{o1}]$$

$\because \beta_m r_o \gg 1$

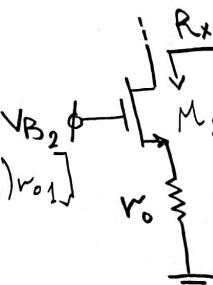

$$\therefore R_{LFD2} = r_{o2} [(\beta_m + \beta_{mb}) r_{o1}] = \beta_m \cdot r_o^2$$

↓  
neglect the Body effect      ∵  $r_{o1} = r_{o2}$


$$\therefore R_x = \beta_m r_o^2 \#$$

## Quiz (2): Lecture (6)

★ Quiz on:  
"hooking from source"

- Assume  $M_1$  and  $M_2$  have the same  $r_o$ ,  $\delta_m r_o \gg 1$ , and neglect body effect.
- Find  $R_x$

Sol.

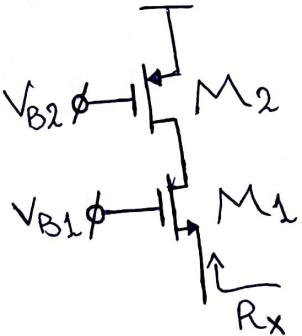

for  $M_1$ :

$$\rightarrow R_x = R_{LFS_1}$$

$$R_{LFS_1} = \frac{1}{\delta_m + \delta_{mb}} \left( 1 + \frac{R_{D_1}}{r_o} \right)$$

$$\cdot R_{D_1} = R_{LFD_2}$$

for  $M_2$ :

$$\rightarrow R_{LFD_2} = r_o \left[ 1 + (\delta_m + \delta_{mb}) R_{S_2} \right]$$

★ Active Load: as the Gate & the Source are AC short circuit

$$\therefore R_x = \frac{1}{\delta_m + \delta_{mb}} \left( 1 + \frac{r_o}{r_o} \right)$$

↓  
neglect body effect

$$\therefore R_x = \frac{2}{\delta_m} \quad \#$$

### Quiz (3): lecture (6)

- Assume  $M_1, M_2$ , and  $M_3$  have the same  $\delta_m$  and  $r_o$ ,  $\delta_m r_o \gg 1$ , and neglect body effect

- Find  $R_x$

Sol.

For  $M_3$ :

$$\rightarrow R_1 = R_{LFD} \rightarrow (\text{active load}) \\ \therefore R_1 = r_o$$

for  $M_2$ :

$$\rightarrow R_2 = R_{LFD} = r_o (1 + (\delta_m + \delta_{mb})) R_s \\ \therefore R_2 = r_o (1 + \delta_m r_o) \quad \begin{matrix} \text{neglect body} \\ \text{effect} \end{matrix}$$

$$\because \delta_m r_o \gg 1$$


$$\therefore R_2 = \delta_m r_o^2$$

for  $M_1$ :

$$\rightarrow R_x = R_{LFS} = \underbrace{\frac{1}{\delta_m + \delta_{mb}}}_{\delta_m r_o^2} \left( 1 + \frac{R_{D1}}{r_o} \right)$$

$$\therefore \frac{R_{D1}}{r_o} = \underbrace{\frac{\delta_m r_o^2}{r_o}}_{\delta_m r_o^2}$$
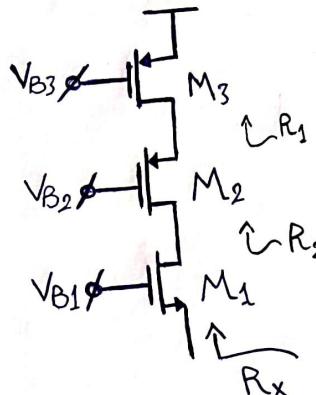
$$\therefore R_x = \frac{1}{\delta_m} (1 + \delta_m r_o) = \frac{1}{\delta_m} (\delta_m r_o) = r_o \#$$



## Quiz(4): Lecture(6)

\* Quiz on:  
"Common Source Amplifier"

- The Circuit below shows a CS amplifier with diode-connected load
- Find the Gain w/  $G_m R_{out}$  (ignore body effect and CLM).
- Express the Gain in terms of  $(W/L)_1$  and  $(W/L)_2$ .
- This is a "Linear" CS amplifier.

Sol.

$$A_v = G_m R_{out}$$



first for  $M_2$  when deactivating  $V_B$

Gate & Drain are connected

So, Diode connected

$$G_m = \frac{-g_m}{1 + g_m R_S}$$

$R_S = 0$

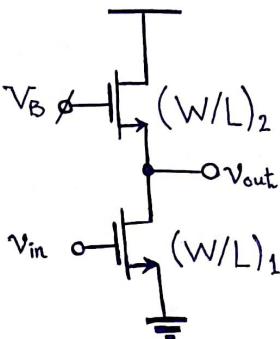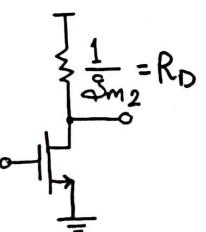

$$\therefore G_m = -g_m$$

$$R_{out} = \frac{1}{g_m} \parallel r_o \approx \frac{1}{g_m}$$

$$A_v = -\frac{g_m}{g_m} = -\frac{\sqrt{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 2I_D}}{\sqrt{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 2I_D}}$$

$$\therefore A_v = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \#$$

## Quiz(5): Lectur(6)

- The circuit below shows a complementary CS amplifier (inverter amp).
- Find the Gain using  $G_m R_{out}$ .



Sol:

By Applying Superposition theorem:

① Deactivate  $V_{in}$  for  $M_2$

$$A'_v (\text{for } M_2) = G'_m R'_{out}$$
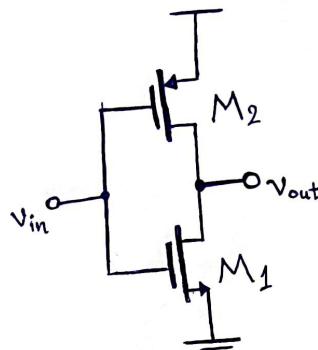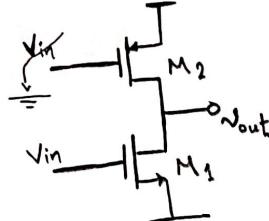
$$\begin{aligned} G'_m &= \frac{-g_{m_1}}{(1 + (g_{m_1} + g_{m_2}) R_{S_1})} \\ &= -g_{m_1} \end{aligned}$$




$$\therefore A'_v (\text{for } M_2) = -g_{m_1} * R'_{out}, R'_{out} = r_{o_1} // r_{o_2}$$

$$A'_v = -g_{m_1} (r_{o_1} // r_{o_2})$$

② Deactivate  $V_{in}$  for  $M_1$

$$A''_v (\text{for } M_1) = G''_m R''_{out}$$
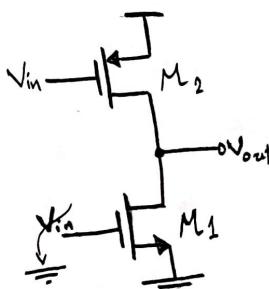
$$\begin{aligned} G''_m &= \frac{-g_{m_2}}{(1 + (g_{m_1} + g_{m_2}) R_{S_2})} \\ &= -g_{m_2} \end{aligned}$$



$$\therefore R''_{out} = r_{o_1} // r_{o_2}$$

$$\therefore A''_v = -g_{m_2} (r_{o_1} // r_{o_2})$$

Sum ① & ②

$$\therefore A_v = -(g_{m_1} + g_{m_2}) (r_{o_1} // r_{o_2})$$

وَمَا أُوتِيتُهُ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

Allah almighty said in the Qur'an :  
“and you 'O humanity' have been given but little knowledge.”

لَوْأَنَ النَّاسَ كُلُّهُمْ سَتَّصِبُوا بِأَمْرٍ اتَرَكُوهُ مَا قَامَ لِلنَّاسِ وَنِيَّا وَلَوْعَنْ

The Muslim Caliph Umar ibn Abdulaziz, May Allah have mercy on him, Said:  
“If every time people found something difficult, they abandoned it, then  
neither worldly affairs nor religion would have ever been established for  
people.”

- All Credits for these lectures go to **Dr. Hesham Omran**, Associate Professor at Ain Shams University and CTO at Master Micro, May Allah bless Dr. Hesham for these Lectures.

<https://www.master-micro.com/professional-courses/analog-ic-design>



- These Notes were made by: **Fady Sabry Negm** and any success or guidance is from Allah, and any mistake or lapse is from me and Satan.