

Analog IC Design

Lecture 02 Review on Circuits and Systems Basics

Dr. Hesham A. Omran

Integrated Circuits Lab (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

وَمَا أُرْتَبَتْهُ مِنَ الْعِلْمِ إِلَّا قَلَّا




Analog IC Design

Lecture 02 Review on Circuits Basics

Dr. Hesham A. Omran

Integrated Circuits Lab (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

Ohm's Law

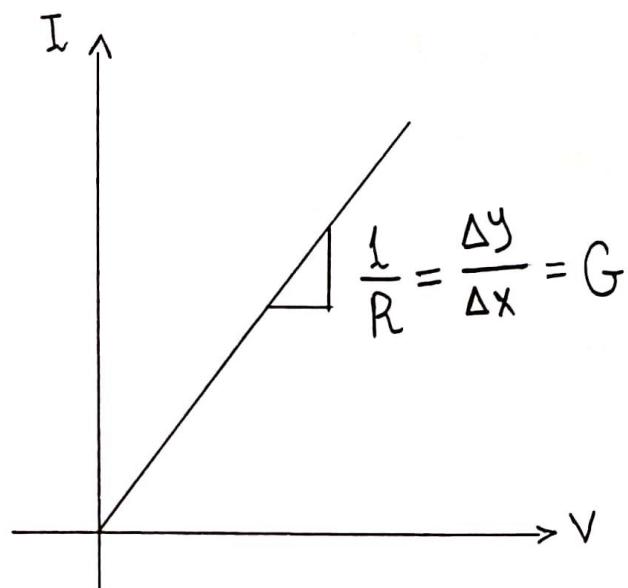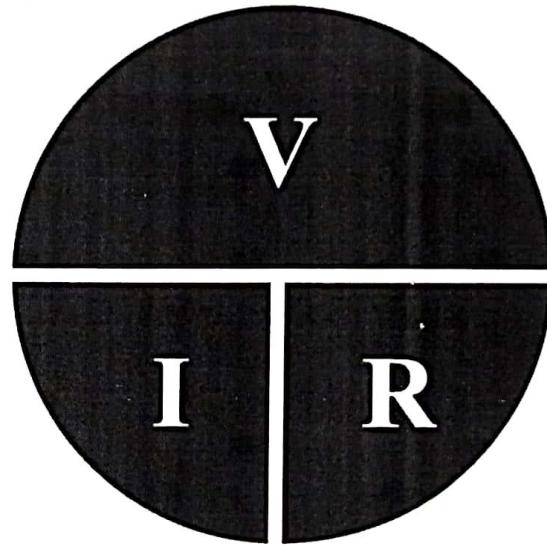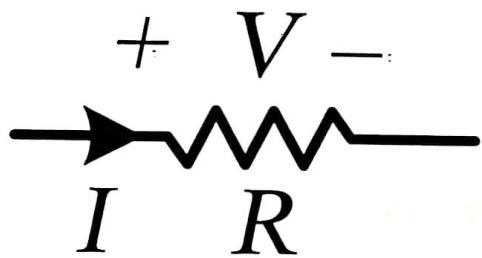


$$V = IR$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$


Kirchhoff's Current Law (KCL)

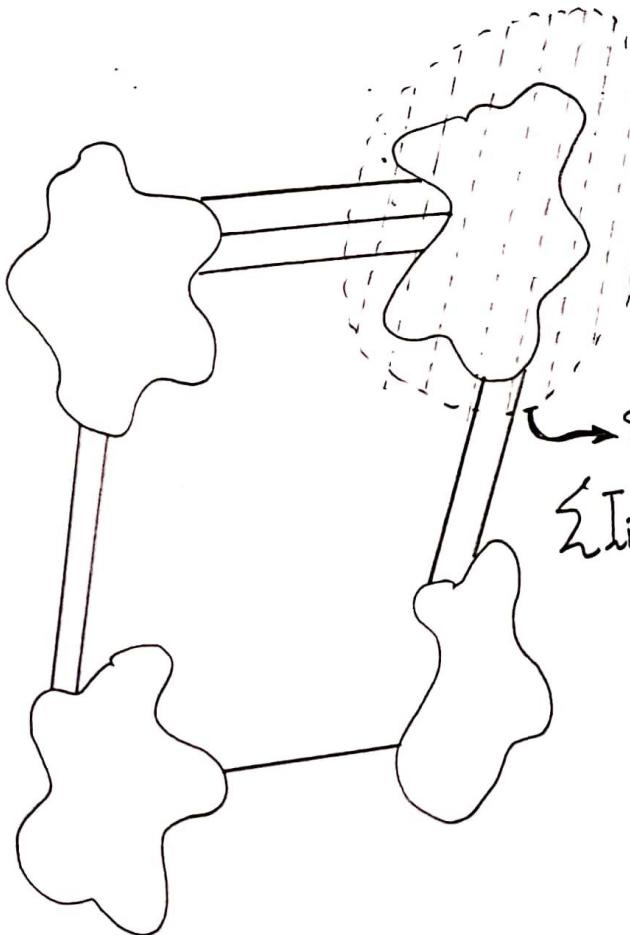- The sum of all currents flowing into a node is zero.



$$\Sigma I = 0$$

$$I_1 + I_2 + I_3 - I_4 = 0$$

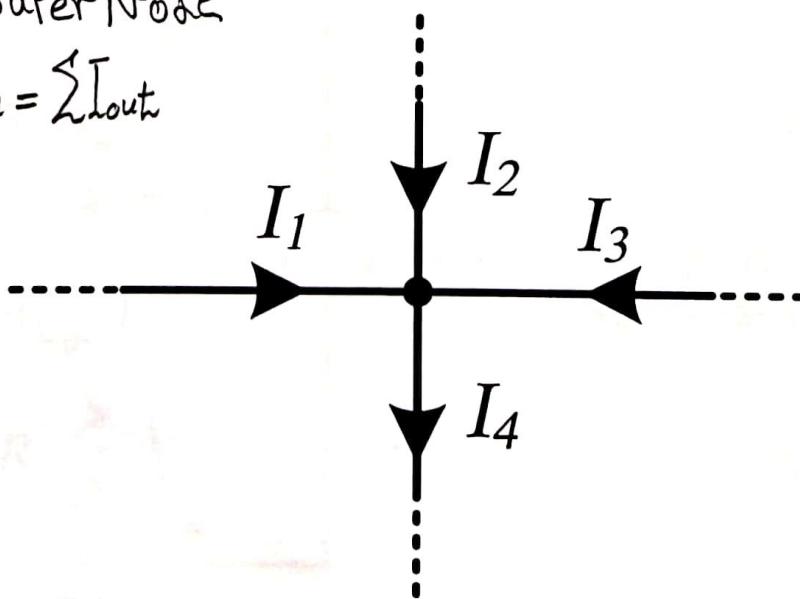



Kirchhoff's Voltage Law (KVL)

- The sum of all voltage drops around any closed loop is zero

$$\Sigma V = 0$$

$$-V_{DD} + I_D R_D + V_{DS} + I_D R_S = 0$$

$$V_{DD} = I_D (R_D + R_S) + V_{DS}$$

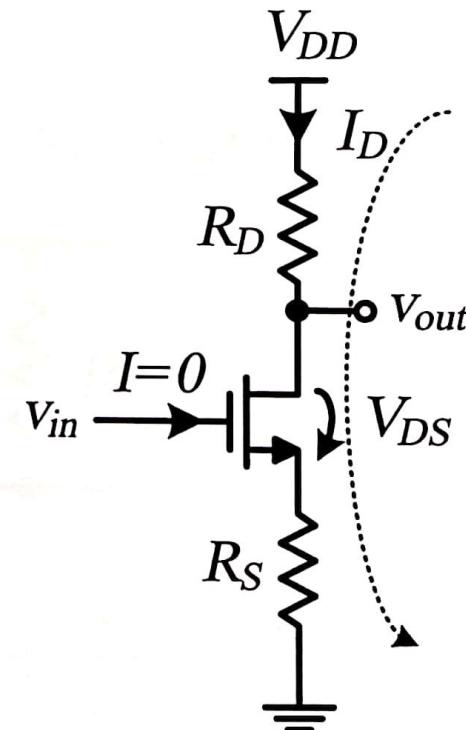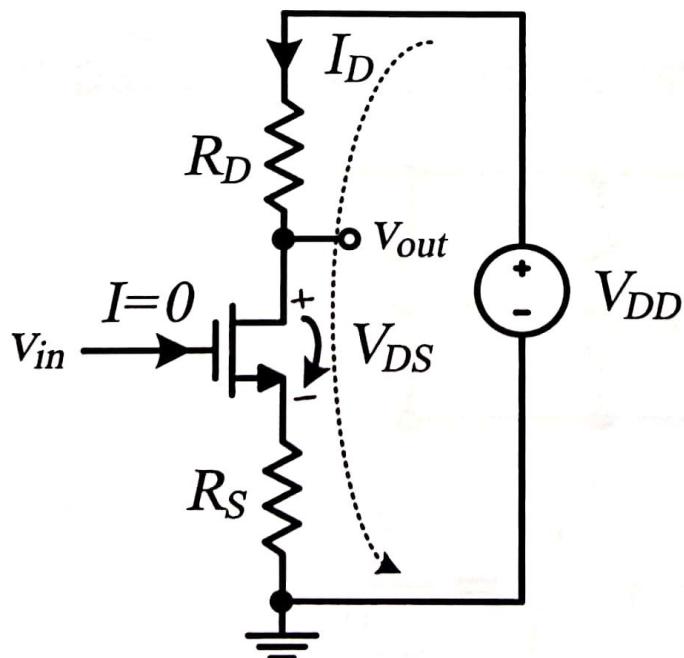


Resistor Combinations

- Resistors in series: Largest resistor dominates



$$R_{eq} = R_1 + R_2 + R_3$$

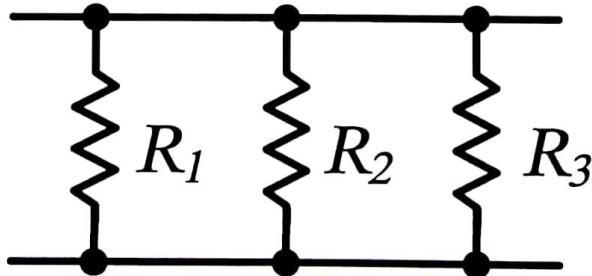- Resistors in parallel: Smallest resistor dominates




$G_{eq} = G_1 + G_2 + \dots$

equivalent conductance

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Voltage and Current Dividers

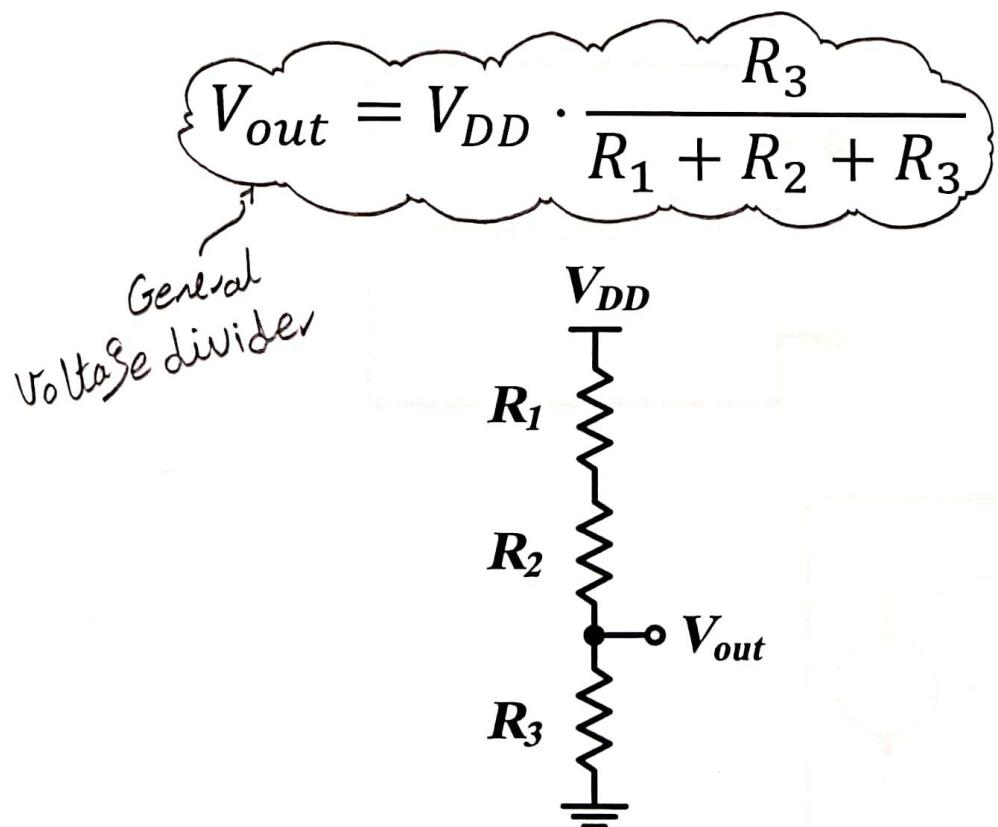- Voltage divider → the largest resistor takes most of the voltage
- Current divider → the smallest resistor (largest conductance) takes most of the current
 - Remember that current flows in the least resistance path



General Current Divider



$$I_{out} = I_{in} \cdot \frac{G_3}{G_1 + G_2 + G_3}$$

Thevenin Equivalent Circuit

- Any one port circuit can be replaced by a voltage source and a series impedance

$$V_{TH} = V_{o.c.}$$
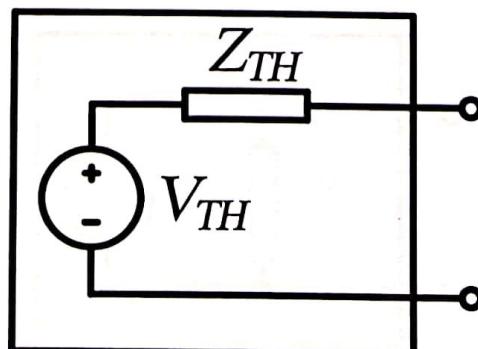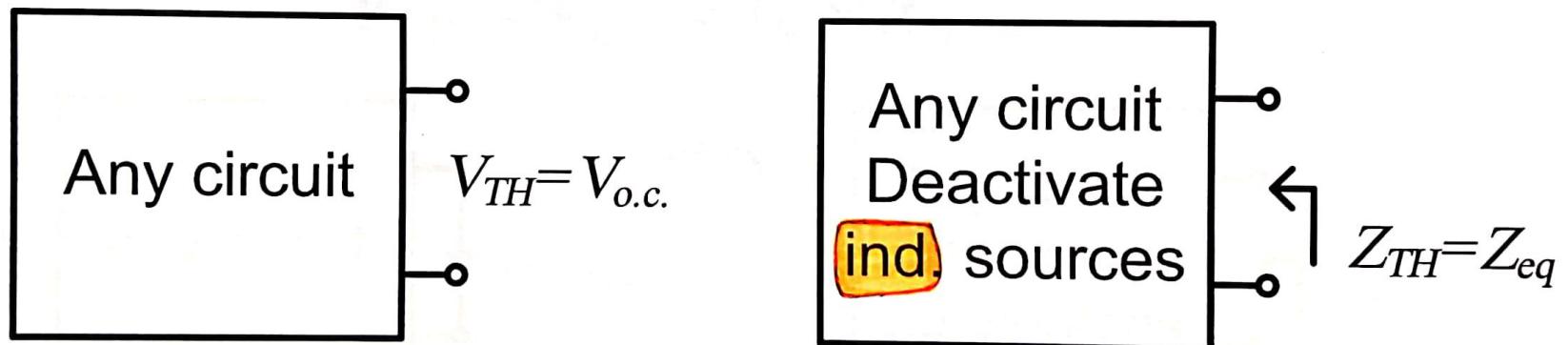
$$Z_{TH} = Z_{eq} \text{ (turn OFF all independent sources)}$$



Norton Equivalent Circuit




- Any one port circuit can be replaced by a current source and a parallel impedance

$$I_N = I_{s.c.}$$

$$Z_N = Z_{eq} \text{ (turn OFF all independent sources)}$$

$$Z_N = Z_{TH}$$

$$V_{TH} = V_{o.c.} = I_N \times Z_N$$

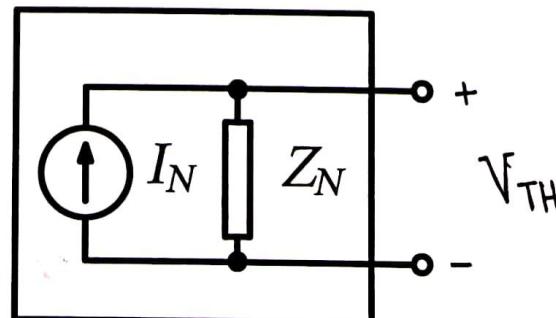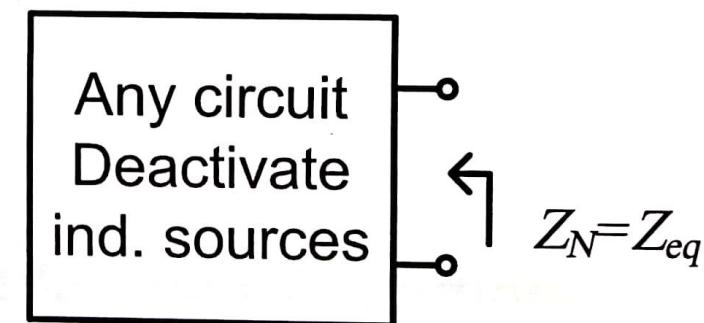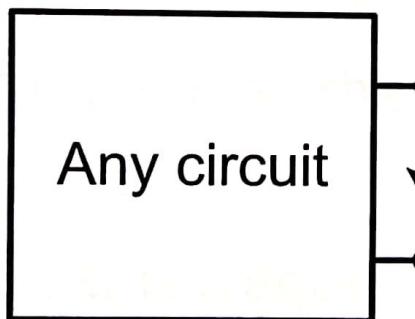

Superposition Theorem

- Deactivate all **independent** sources except one
 - Independent voltage source → short circuit (s.c.)
 - Independent current source → open circuit (o.c.)
 - Do NOT deactivate dependent sources
- Solve the circuit
- Repeat the previous two steps for every source
- Algebraically add all the results

$$V_o = V'_o + V''_o + V'''_o$$

We use this frequently to separate AC and DC solutions

*for this theorem
to be valid circuit should
be linear.

Superposition Theorem

DC + AC

=




DC Analysis
or DC equivalent circuit

DC

+

AC Analysis
or AC equivalent circuit

AC

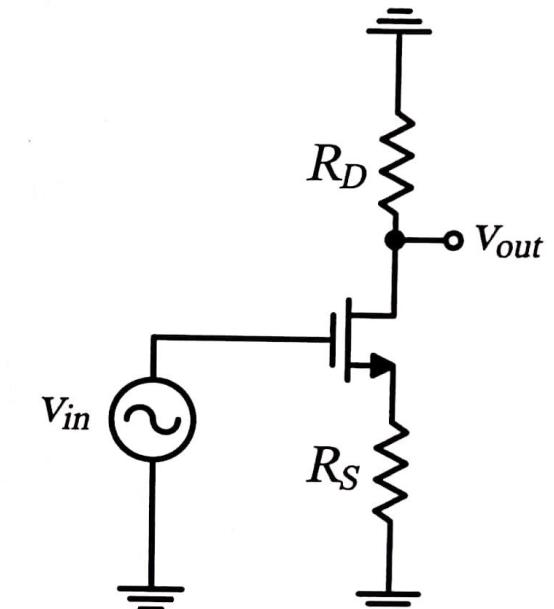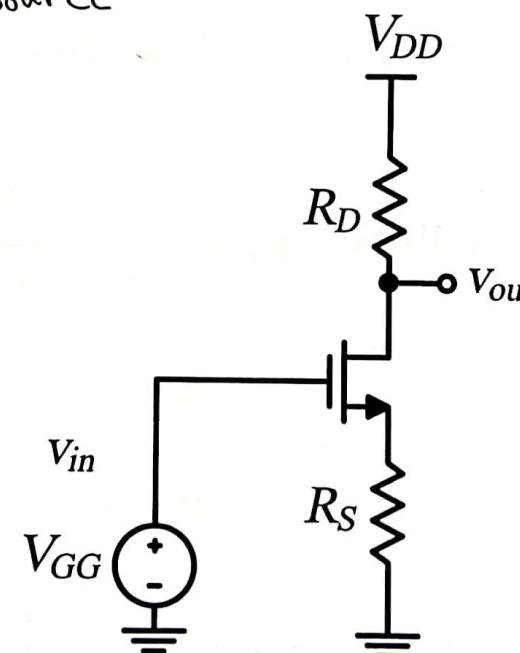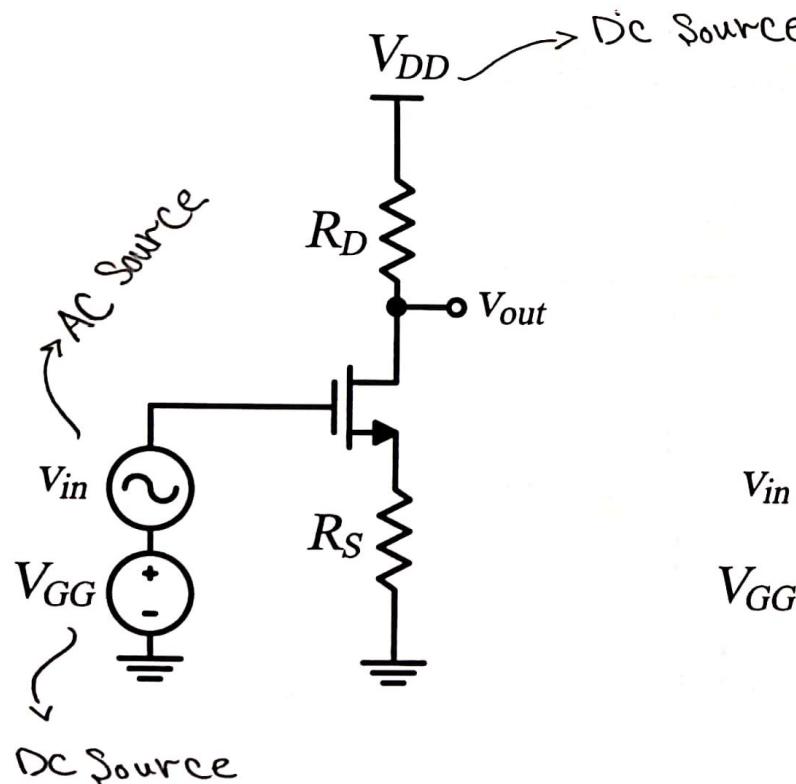

Capacitance

$$Q = CV$$

$$i = \frac{dQ}{dt} = C \frac{dV}{dt} \xrightarrow{\cos(\omega t) + j\omega \sin(\omega t)}$$

$$V = V_0 \cos \omega t = V_0 \cdot \text{Re}\{e^{j\omega t}\} \Rightarrow V_0 e^{j\omega t}$$

$$i = C \frac{dV}{dt} = j\omega C (V_0 e^{j\omega t}) = j\omega C \cdot V$$

We omit "Re" for simplicity


$$Z_C = \frac{V}{i} = \frac{1}{j\omega C} = \frac{1}{sC} \xrightarrow{\text{frequency Domain, "s-Domain", "Laplace", Reactance}} X_C = \frac{1}{\omega C}$$

High frequency

$$\omega \uparrow \uparrow \Rightarrow X_C \rightarrow 0 \Rightarrow s.c.$$


Small frequency
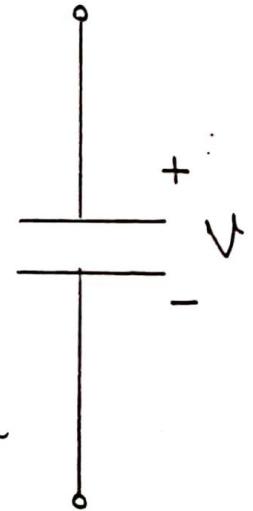
$$\omega \downarrow \downarrow \Rightarrow X_C \rightarrow \infty \Rightarrow o.c.$$



Capacitance Combinations

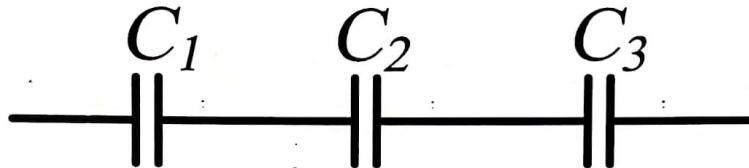
- Capacitors in series: Smallest capacitor dominates



$$X_C = \frac{1}{\omega C}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

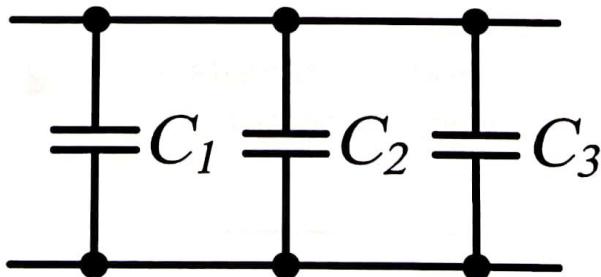- Capacitors in parallel: Largest capacitor dominates



$$C_{eq} = C_1 + C_2 + C_3$$

Laplace Transform (LT)


* Most systems are described by ODE

$$\begin{aligned} Q &= CV \\ i &= \frac{dQ}{dt} \\ &= C \frac{du}{dt} \end{aligned}$$



time domain

Laplace domain

$\delta(t)$ 'impulse signal'

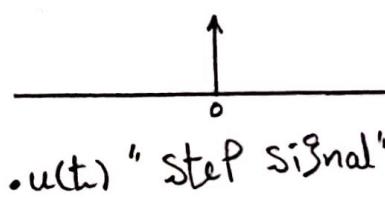

$u(t)$ "step signal"

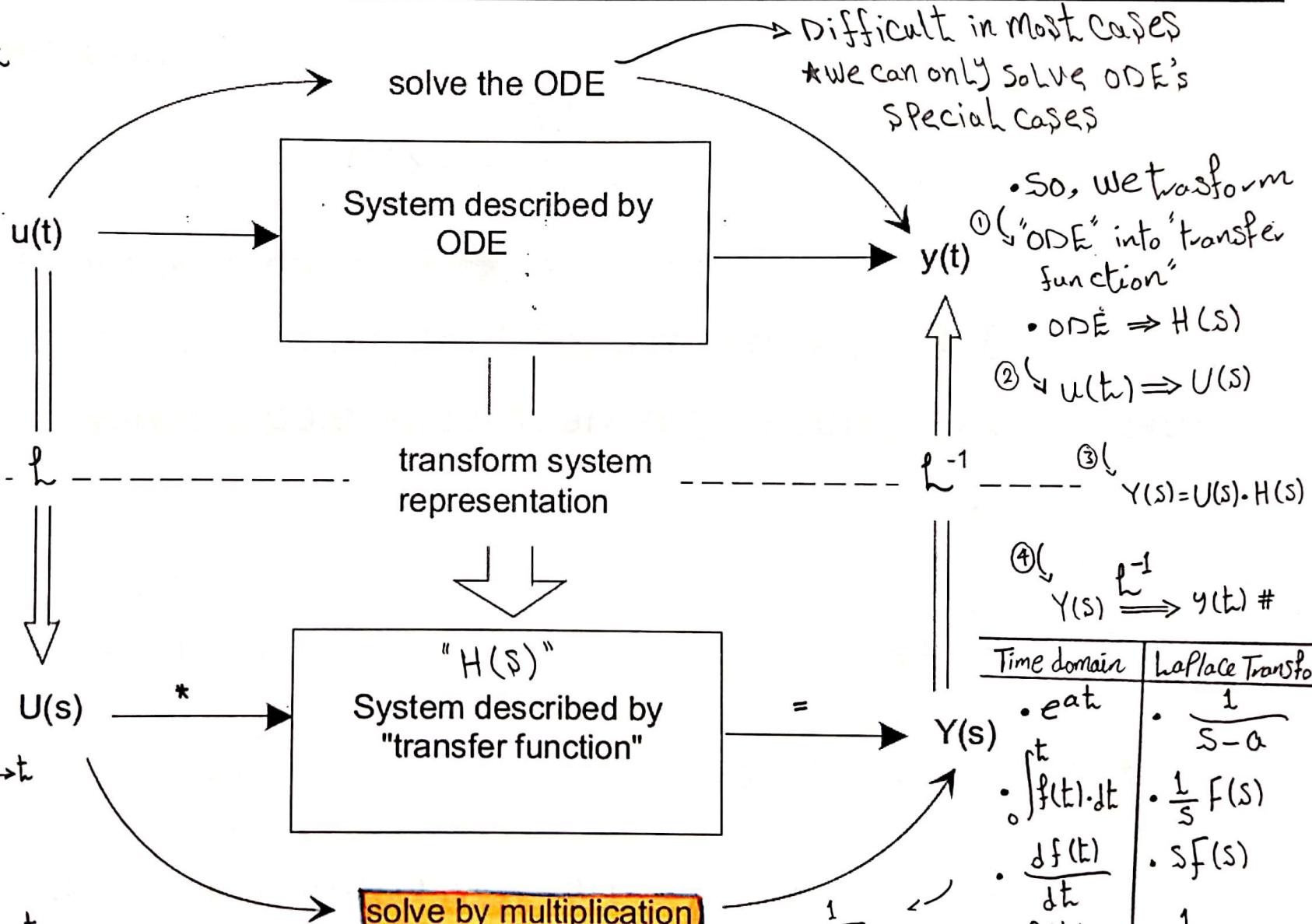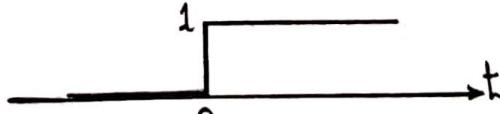


* Actually step function 'u(t)' is the integration of the impulse function 'δ(t)', so, by dividing $L\{u(t)\}$ by 's': $L\{\delta(t)\} = \frac{1}{s}$

Poles and Zeros

*missing two slides
before this one.
03:00 → 09:25


□ Transfer function

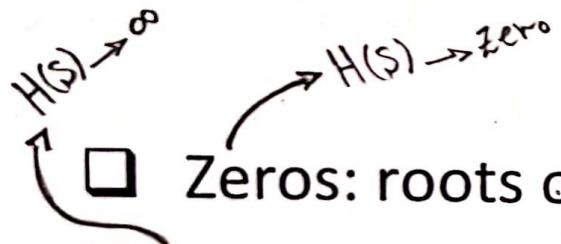

$$H(s) = \frac{N(s)}{D(s)}$$

- Zeros: roots of the numerator $\rightarrow N(s) = 0$
- Poles: roots of the denominator (characteristic eq.) $\rightarrow D(s) = 0$
- For physical systems, poles & zeros are real or complex conjugate
- Example:
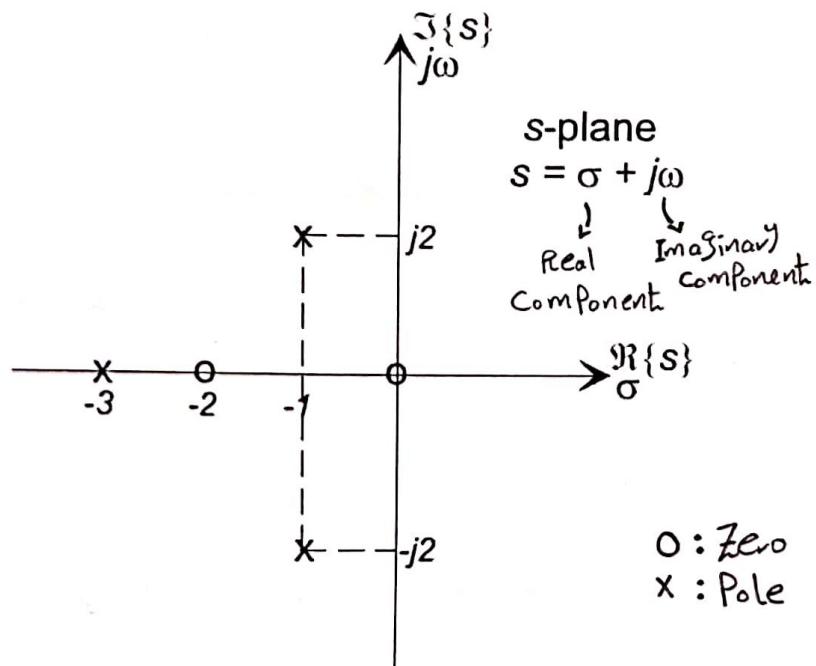
$$\begin{aligned} G(s) &= \frac{5s^2 + 10s}{s^3 + 5s^2 + 11s + 5} \\ &= \frac{5s(s+2)}{(s+3)(s^2 + 2s + 5)} \\ &= \frac{5s(s+2)}{(s+3)(s + (1+j2))(s + (1-j2))} \end{aligned}$$




left half Plane


Pole-Zero Plot

*missing slide before
this one.
09:25 → 11:50

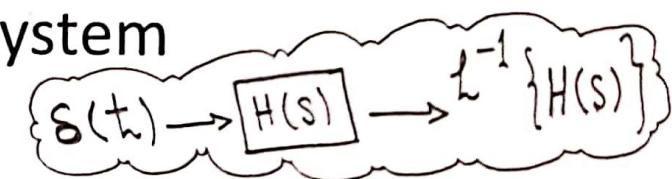- Poles in LHP: Decaying exponential → Stable system
 - BIBO: Bounded input bounded output



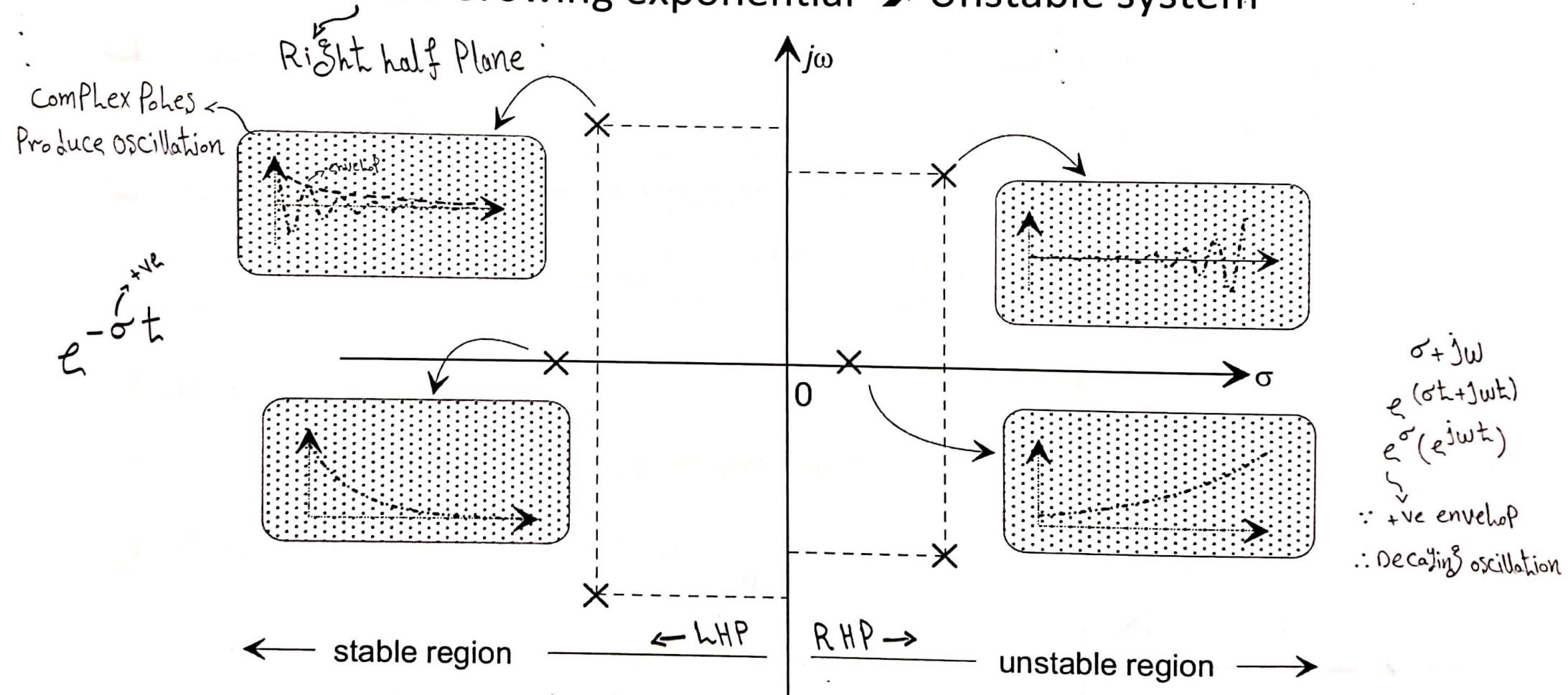- Poles in RHP: Growing exponential → Unstable system



$\sigma + j\omega$
 $e^{(\sigma t + j\omega t)}$
 $e^\sigma (e^{j\omega t})$
↓
+ve envelop
↓
Decaying oscillation

Frequency Response

□ Transfer function

③ 'Frequency Response': if the input is sinusoidal @ specific frequency, then you'll see a magnitude response & phase response.

$$H(s) = \frac{N(s)}{D(s)}$$

$$\textcircled{1} \quad s = \dot{\phi} + j\omega$$

② In circuit, we deliver (transfer) our electricity with Sinusoidal Signal so, Power Engineers considered sinusoidal signal as the steady state so, it's easier.

with sinusoids to write frequency response.

□ Fourier Transform is a special case of Laplace Transform: $s \Rightarrow j\omega$

- $\sigma = 0 \rightarrow$ Steady state response for sinusoidal input

□ Transfer function → Frequency response: $s \Rightarrow j\omega$

$$\frac{1}{a+jb} = \frac{1}{r} e^{-j\theta}$$


$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = |H(j\omega)| e^{j\phi}$$

freq. response magnitude phase


$a + jb = re^{j\theta}$

$r = \text{Magnitude}(a + jb) = \sqrt{a^2 + b^2}$

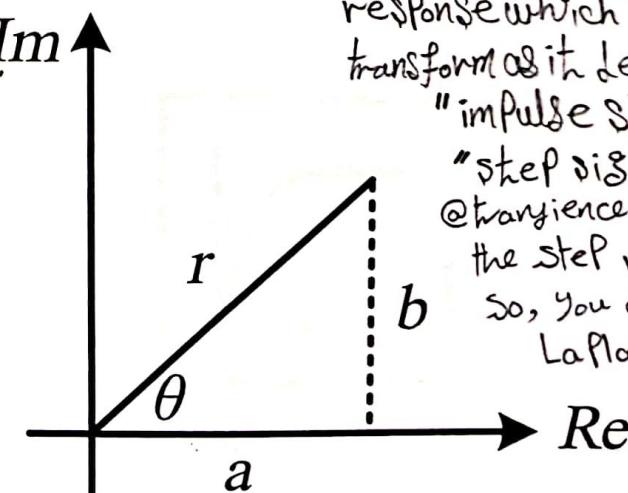$\theta = \text{Phase}(a + jb) = \tan^{-1} \frac{b}{a}$



* Laplace is used in transient

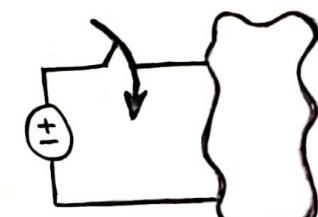

* this is a transient response which fits Laplace transform as it deals with "impulse signal"


"step signal"
@ transience you see the step response so, you deal with Laplace.

Frequency Response

- Y-axis: magnitude of frequency response, x-axis: frequency


LPF

Low Pass Response

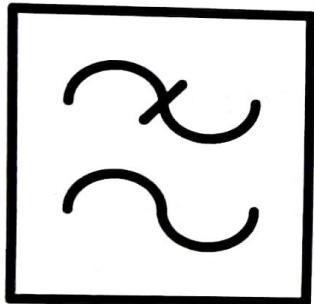





BPF

Band-Pass filter

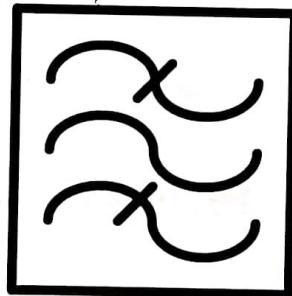

HPF

High Pass response

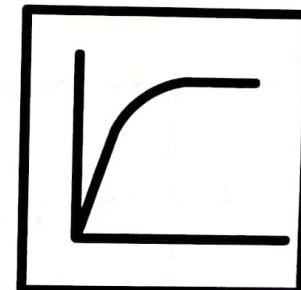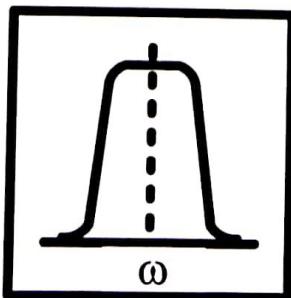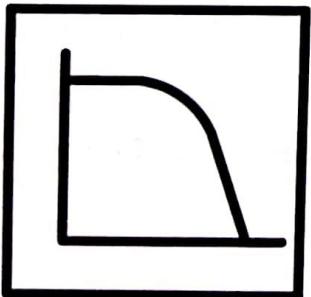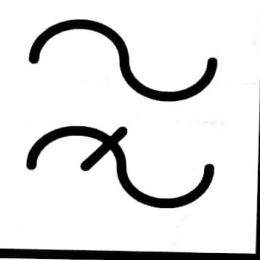

* Actually there is no system that have a high pass response extended to infinity, @ some point it must go down to zero as : every system have a capacitance and the capacitance @ infinity is a short circuit.

1st Order LPF

③ ★ no. of zeroes should be equal to no. of poles.
So, where is the zero? ↗

$$H(s) = \frac{v_{out}(s)}{v_{in}(s)} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC} = \frac{1}{(1 + s\tau)}$$

Voltage Divider

Transfer function
or Frequency response

$$H(j\omega) = \frac{v_{out}(j\omega)}{v_{in}(j\omega)} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\frac{\omega}{\omega_c}}$$

1 → ≠ 0 so, no zeroes?

= 0 → 1 Pole
@ $s = -\frac{1}{\tau}$

$\frac{1}{\tau} = \omega_c$

□ $\tau = RC$: time constant

④ ★ $\omega_c = \frac{1}{RC} \rightarrow \frac{1}{time} = \text{angular freq.}$

□ $\omega_c = \frac{1}{\tau} = \frac{1}{RC}$: cutoff/corner frequency

□ Poles: $s_p = -\frac{1}{\tau} = -\omega_c$ → Pole frequency

doesn't affect the freq. response or the transfer func. as we won't see it.

□ Zeros: ? $\xrightarrow{5} c = \frac{1}{j\omega_c}$ → magnitude



⑥ $\omega \rightarrow \infty, \therefore s_z = \infty$

where ④ is the zero?
the zero is the third □ which makes the transfer function = 0
 $\therefore V_{out} = 0$
this happens when $C = S.C.$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

Phase


as Complex No. is in the denominator

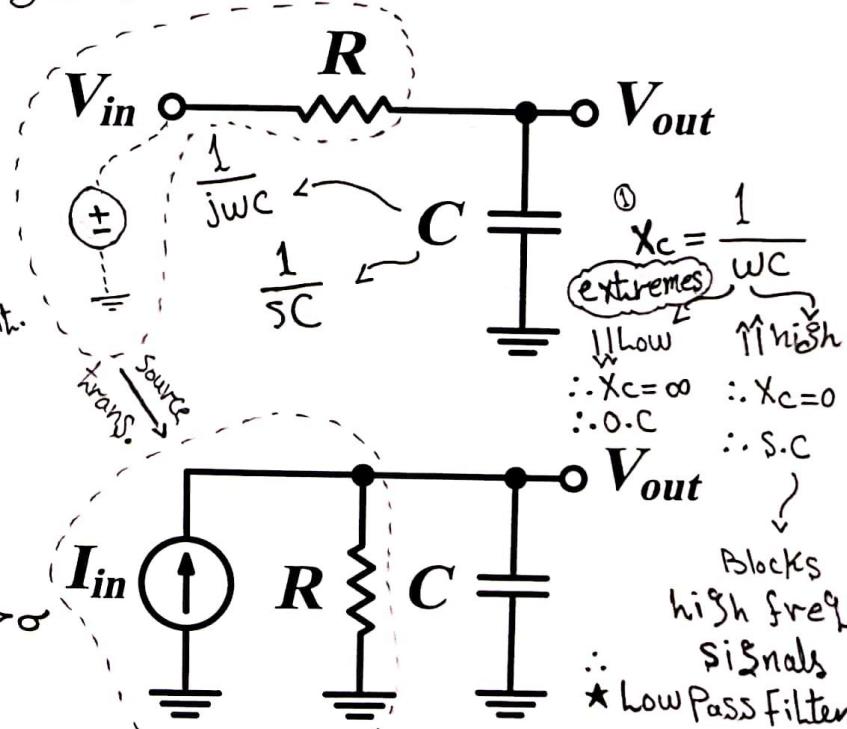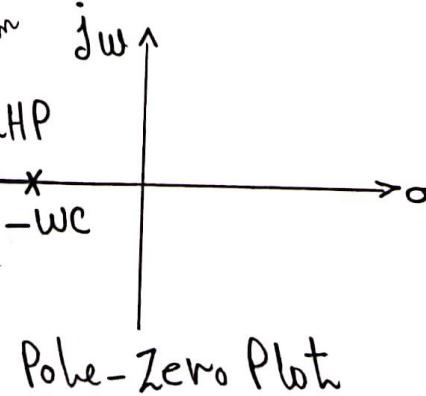

* to plot frequency response

Bode Plot Rules

	Pole	Zero
Magnitude	$-20 \text{ dB/decade} \rightarrow *^{10}$ Actual Mag @ pole: -3 dB	$+20 \text{ dB/decade}$ Actual Mag @ zero: +3 dB
Phase	$-90^\circ \rightarrow$ to be stable system Actual Phase @ pole: -45°	LHP zero: $+90^\circ$ Actual Phase @ zero: $+45^\circ$ RHP zero: -90° Actual Phase @ zero: -45°

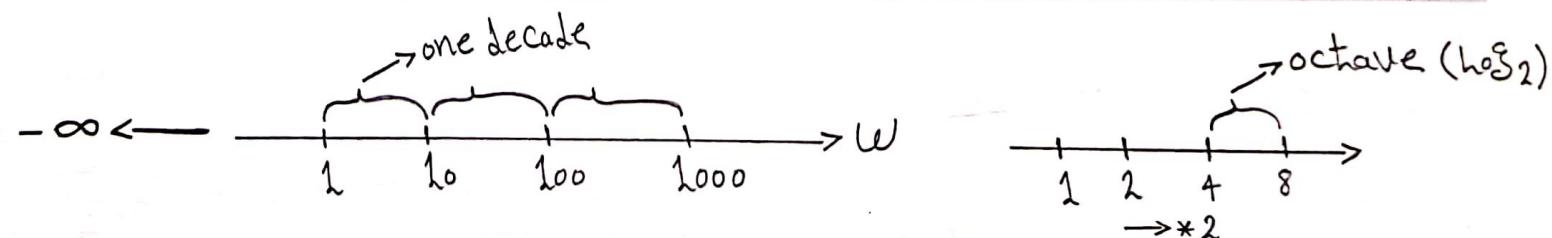


- RHP: Right-half plane ($Re\{s\} > 0$)
- LHP: Left-half plane ($Re\{s\} < 0$)

1st Order LPF Bode Plot

missing 1 next slide

36:36 → 38:49


$20 \log|H(j\omega)|$ (dB)

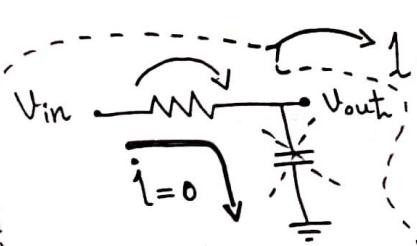

@ low frequency


after corner frequency

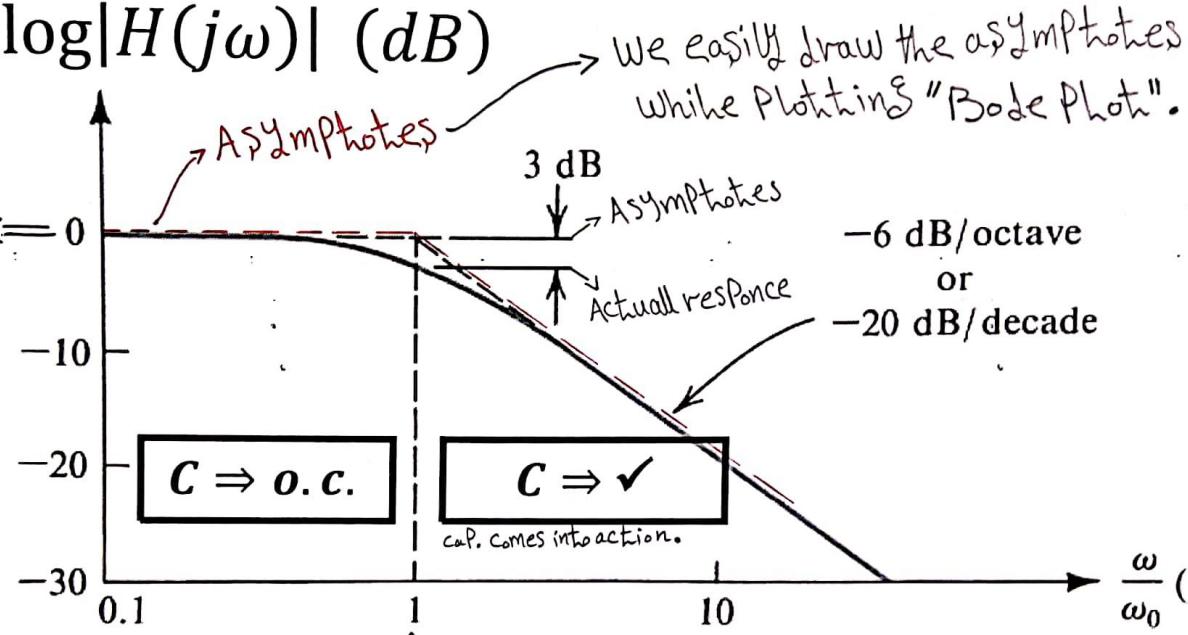* cap. will have small impedance and will pull the output towards the ground, so the response will be zero
(@ infinite frequency)




$P(H(j\omega))$ (a)

$$\omega = \omega_c = \omega_0$$

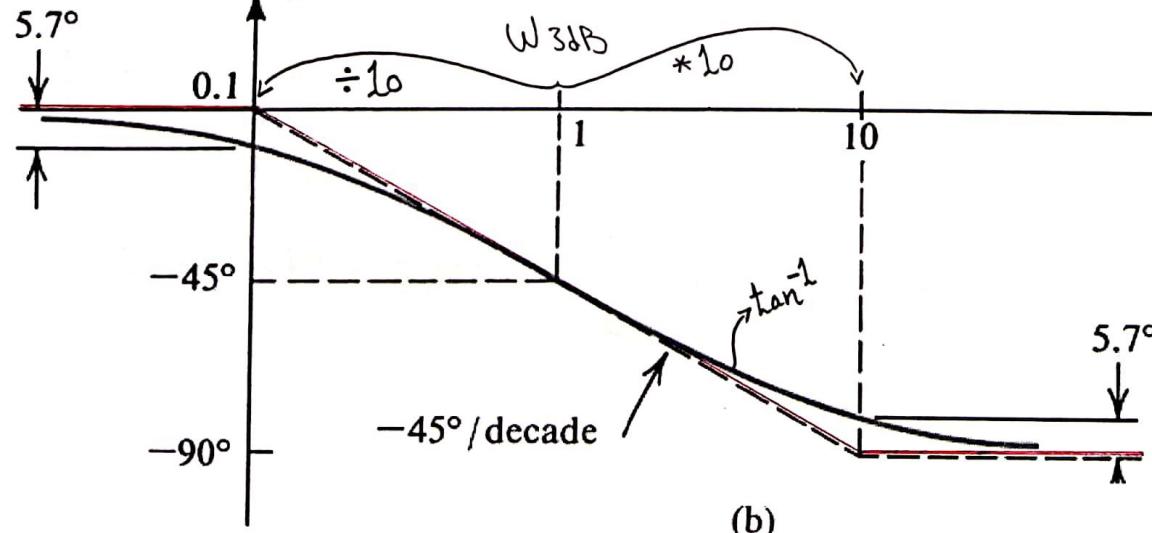

(b)

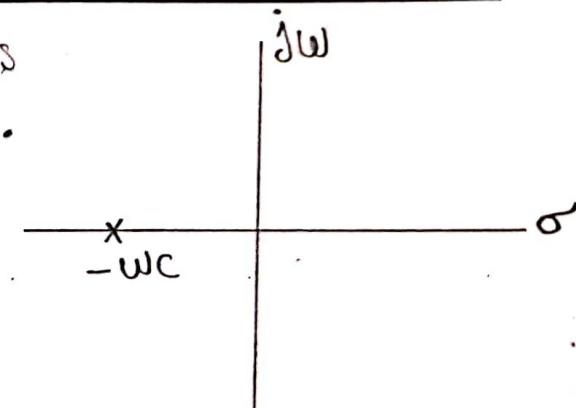

$$A \sin \omega t \xrightarrow{\text{LTI}} \frac{A}{\sqrt{2}} \sin(\omega t - 45^\circ)$$

ω_x

* no change in ω_x only in magnitude & phase

1st Order HPF

$$H(s) = \frac{v_{out}(s)}{v_{in}(s)} = \frac{R}{R + 1/sC} = \frac{sRC}{1 + sRC} = \frac{s\tau}{1 + s\tau}$$



$$H(j\omega) = \frac{v_{out}(j\omega)}{v_{in}(j\omega)} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC} = \frac{\frac{j\omega}{\omega_c}}{1 + \frac{j\omega}{\omega_c}}$$

Poles: $s_p = -\frac{1}{\tau} = -\omega_c$


Zeros: $s_z = 0$

$|H(j\omega)| = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$

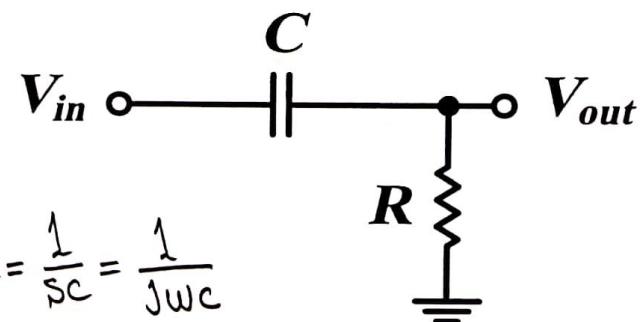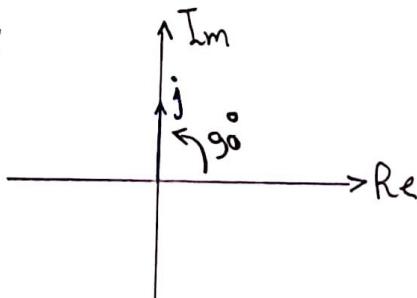$P(H(j\omega)) = 90^\circ - \tan^{-1} \frac{\omega}{\omega_c}$



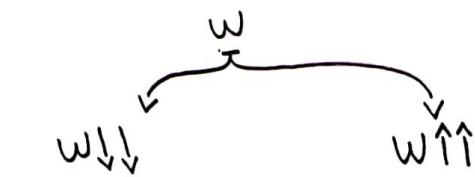* $C = \frac{1}{sC} = \frac{1}{j\omega C}$



\therefore Open circuit
 $\therefore V_{out} \rightarrow 0$

\therefore Short circuit
 $\therefore V_{out} \approx V_{in}$

* if Cap. between
output & GND
↳ shunt output to GND

\therefore LPF
* if Cap. between
i/p & o/p in signal path
 \therefore HPF

Bode Plot Rules

	Pole	Zero
Magnitude	-20 dB/decade Actual Mag @ pole: -3 dB	+20 dB/decade Actual Mag @ zero: +3 dB
Phase	-90° Actual Phase @ pole: -45°	LHP zero: +90° Actual Phase @ zero: +45° RHP zero: -90° Actual Phase @ zero: -45°




- RHP: Right-half plane ($Re\{s\} > 0$)
- LHP: Left-half plane ($Re\{s\} < 0$)

1st Order HPF Bode Plot

→ missing 4 slides "next"

45:05 → end


$20 \log|H(j\omega)|$ (dB)

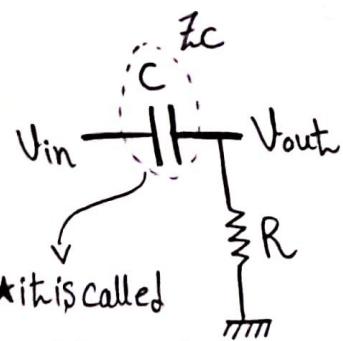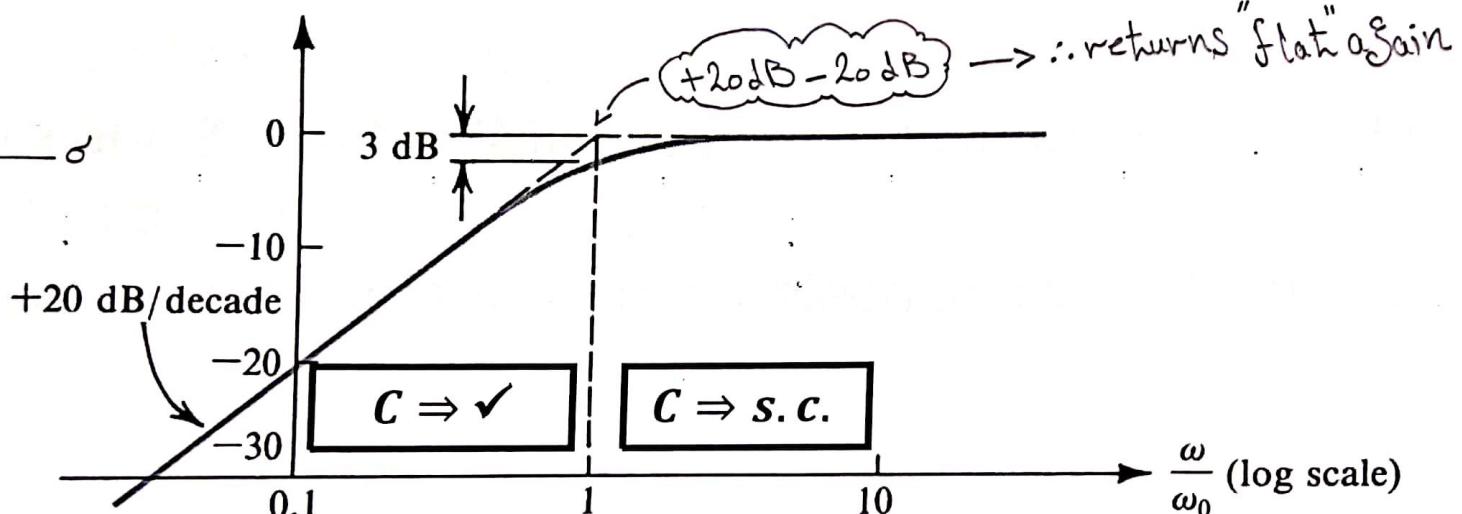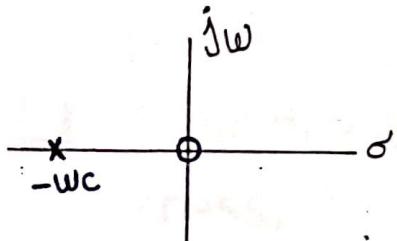

* it is called DC Blocking Capacitor as it makes a complete blocking @ zero frequency.
"Open circuit"

$P(H(j\omega))$
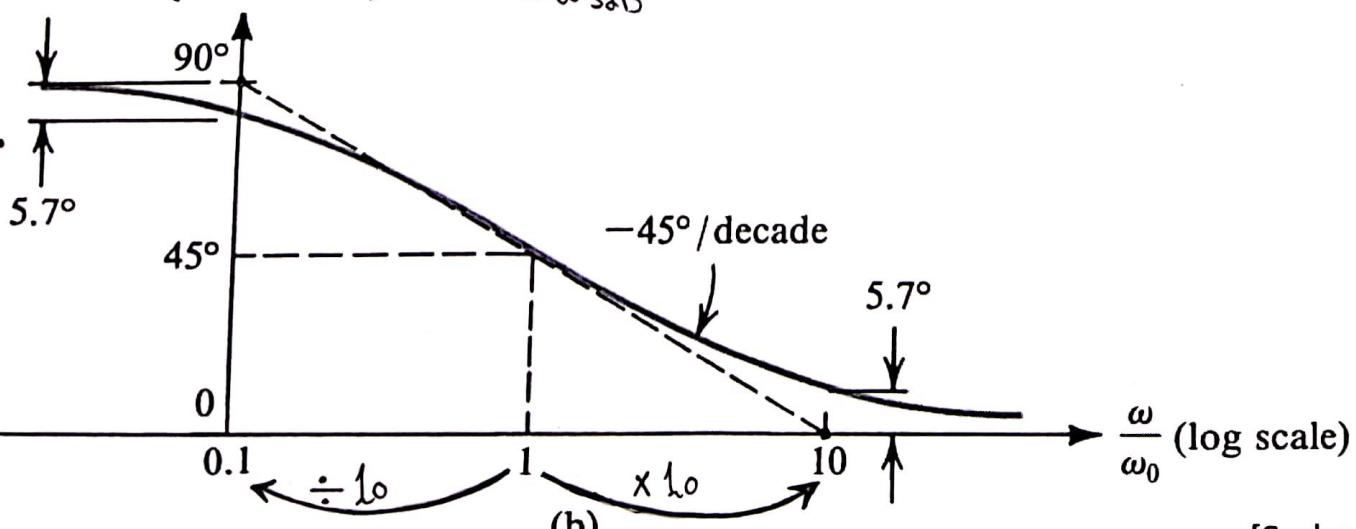
$$\omega = \omega_c = \omega_0 = \omega_p \text{ (a)} \\ = \omega_{-3dB}$$



References

- T. Floyd and D. Buchla, "Electronics Fundamentals, Circuits, Devices, and Applications," 8th ed., Pearson, 2014
- A. Sedra and K. Smith, "Microelectronic circuits," Oxford University Press, 7th ed., 2015
- B. Razavi, "Fundamentals of microelectronics," 2nd ed., Wiley, 2014

Thank you!

Dr. Hesham Omran's Lectures
Fady Sabry Negm's Notes

وَمَا أُوتِيتُهُ مِنَ الْعِلْمِ إِلَّا قَلِيلًا

Allah almighty said in the Qur'an :
“and you 'O humanity' have been given but little knowledge.”

لَوْأَنَ النَّاسَ كُلُّهُمْ سَتَّصِبُوا بِأَمْرٍ اتَرَكُوهُ مَا قَامَ لِلنَّاسِ وَنِيَّا وَلَوْعَنْ

The Muslim Caliph Umar ibn Abdulaziz, May Allah have mercy on him, Said:
“If every time people found something difficult, they abandoned it, then
neither worldly affairs nor religion would have ever been established for
people.”

- All Credits for these lectures go to **Dr. Hesham Omran**, Associate Professor at Ain Shams University and CTO at Master Micro, May Allah bless Dr. Hesham for these Lectures.

<https://www.master-micro.com/professional-courses/analog-ic-design>



- These Notes were made by: **Fady Sabry Negm** and any success or guidance is from Allah, and any mistake or lapse is from me and Satan.